

Example 1

A 50 m long copper wire ($\rho = 1.72 \times 10^{-8} \Omega \cdot \text{m}$) has a diameter of 1.0 mm and is connected to a 6 V. Find:

- the resistance of the wire.
- the current through the wire.

Example 1:


$$\ell = 50 \text{ m}, D = 1.0 \text{ mm}, \Delta V = 6 \text{ V}, \text{ and } \rho = 1.72 \times 10^{-8} \Omega \cdot \text{m}$$

a.) $R = ?$

$$R = \frac{\rho \ell}{A} = \frac{\rho \ell}{\pi r^2} = \frac{(1.72 \times 10^{-8} \Omega \cdot \text{m})(50 \text{ m})}{\pi (0.5 \times 10^{-3} \text{ m})^2}$$

$$R = 1.1 \Omega$$

b.) $I = ?$

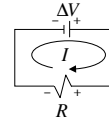

$$\Delta V = IR$$

$$I = \frac{\Delta V}{R} = \frac{6 \text{ V}}{1.1 \Omega}$$

$$I = 5.45 \text{ A}$$

Example 2:


A 24Ω resistor is connected to a 6.0 V battery.

- Find the current through the resistor.
- Find the power delivered to the resistor.
- How much energy is dissipated in the resistor in 1.0 hour?

Example 2:

$$R = 24 \Omega \text{ and } \Delta V = 6.0 \text{ V}$$

a.) $I = ?$

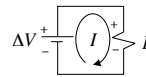

$$\Delta V = IR$$

$$I = \frac{\Delta V}{R} = \frac{6.0 \text{ V}}{24 \Omega}$$

$$I = 0.25 \text{ A}$$

b.) $P = ?$

$$P = I\Delta V = (0.25 \text{ A})(6.0 \text{ V}) \quad P = I^2 R = (0.25 \text{ A})^2 (24 \Omega) = 1.5 \text{ W}$$

$$P = 1.5 \text{ W}$$

$$P = \frac{\Delta V^2}{R} = \frac{(6.0 \text{ V})^2}{24 \Omega} = 1.5 \text{ W}$$

c.) $t = 1 \text{ h}, E = ?$

$$E = Pt = (1.5 \text{ W})(3600 \text{ s})$$

$$E = 5400 \text{ J}$$


Example 3:

A 120Ω , a 60Ω , and a 40Ω resistor are connected in series with a 110 V power source.

- Draw a schematic diagram.
- What is the equivalent resistance of the circuit?
- What is the current from the power source?
- What is the current through each resistor?
- What is the voltage drop across each resistor?

Example 3: $R_1 = 120 \Omega, R_2 = 60 \Omega, R_3 = 40 \Omega$, and $\Delta V = 110 \text{ V}$

a.) schematic diagram in series

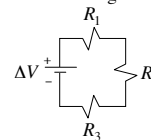

b.) $R_{eq} = ?$

$$R_{eq} = R_1 + R_2 + R_3$$

$$R_{eq} = 120 \Omega + 60 \Omega + 40 \Omega$$

$$R_{eq} = 220 \Omega$$

c.) $I = ?$

$$\Delta V = IR_{eq} \quad I = \frac{\Delta V}{R_{eq}} = \frac{110 \text{ V}}{220 \Omega}$$

$$I = 0.50 \text{ A}$$

d.) I 's = ? for each resistor

Resistors in series have the same current and the same current as their equivalent so:

$$I_1 = I_2 = I_3 = I = 0.50 \text{ A}$$

e.) ΔV 's = ? for each resistor

$$\Delta V_1 = I_1 R_1$$

$$\Delta V_2 = I_2 R_2$$

$$\Delta V_3 = I_3 R_3$$

$$\Delta V_1 = (0.5 \text{ A})(120 \Omega) \quad \Delta V_2 = (0.5 \text{ A})(60 \Omega) \quad \Delta V_3 = (0.5 \text{ A})(40 \Omega)$$

$$\Delta V_1 = 60 \text{ V}$$

$$\Delta V_2 = 30 \text{ V}$$

$$\Delta V_3 = 20 \text{ V}$$


Example 4:

A 120 Ω, a 60 Ω, and a 40 Ω resistor are connected parallel to a 110 V power source.

- Draw a schematic diagram.
- What is the equivalent resistance of the circuit?
- What is the current from the power source?
- What is the voltage drop across each resistor?
- What is the current through each resistor?

Example 4 : $R_1 = 120 \Omega$, $R_2 = 60 \Omega$, $R_3 = 40 \Omega$, and $\Delta V = 110 \text{ V}$

a.) schematic diagram in parallel

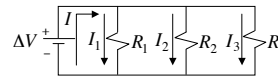

b.) $R_{eq} = ?$

$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

$$R_{eq} = \left(\frac{1}{120 \Omega} + \frac{1}{60 \Omega} + \frac{1}{40 \Omega} \right)^{-1}$$

$$R_{eq} = 20 \Omega$$

c.) $I = ?$

$$\Delta V = IR_{eq}$$

$$I = \frac{\Delta V}{R_{eq}} = \frac{110 \text{ V}}{20 \Omega}$$

$$I = 5.5 \text{ A}$$

d.) V 's = ? for each resistor

Resistors in parallel have the same voltage and the same voltage as their equivalent so :

$$\Delta V_1 = \Delta V_2 = \Delta V_3 = \Delta V = 110 \text{ V}$$

e.) I 's = ? for each resistor

$$I_1 = \frac{\Delta V_1}{R_1} = \frac{110 \text{ V}}{120 \Omega}$$


$$I_1 = 0.9167 \text{ A}$$

$$I_2 = \frac{\Delta V_2}{R_2} = \frac{110 \text{ V}}{60 \Omega}$$

$$I_2 = 1.833 \text{ A}$$

$$I_3 = \frac{\Delta V_3}{R_3} = \frac{110 \text{ V}}{40 \Omega}$$

$$I_3 = 2.75 \text{ A}$$

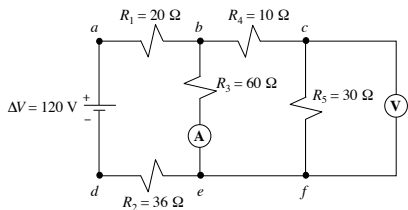


Example 5:


For the circuit shown above:

- Find the equivalent resistance.
- The current and voltage for each resistor.
- The readings on the ammeter and on the voltmeter.
- The voltages V_{ae} and V_{fb} .

Example 5 :

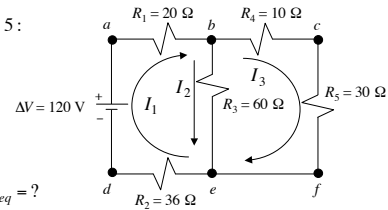


a.) $R_{eq} = ?$

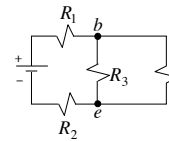

$$R_{4,5} = R_4 + R_5$$


$$R_{4,5} = 10 \Omega + 30 \Omega$$

$$R_{4,5} = 40 \Omega$$

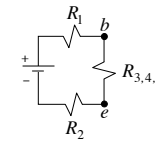

$$R_{3,4,5} = \left(\frac{1}{R_3} + \frac{1}{R_{4,5}} \right)^{-1}$$
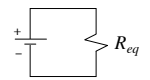
$$R_{3,4,5} = \left(\frac{1}{60 \Omega} + \frac{1}{40 \Omega} \right)^{-1} = 24 \Omega$$




$$R_{eq} = R_1 + R_2 + R_{3,4,5}$$


$$R_{eq} = 20 \Omega + 36 \Omega + 24 \Omega$$

$$R_{eq} = 80 \Omega$$

Example 5 :

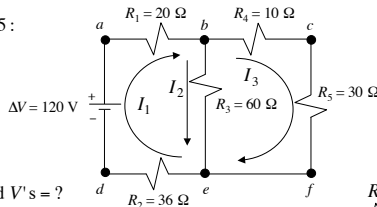

b.) I 's and V 's = ?

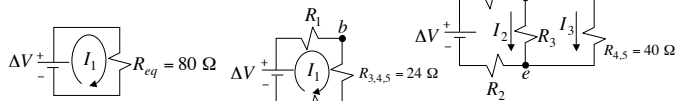

$$I_1 = \frac{\Delta V}{R_{eq}}$$

$$I_1 = \frac{120 \text{ V}}{80 \Omega}$$

$$I_1 = 1.5 \text{ A}$$

$$V_{bc} = I_1 R_{3,4,5}$$

$$V_{bc} = (1.5 \text{ A})(24 \Omega)$$


$$V_{bc} = 36 \text{ V}$$

$$\Delta V_3 = \Delta V_{4,5} = V_{bc} = 36 \text{ V}$$

$$I_2 = \frac{\Delta V_3}{R_3} = \frac{36 \text{ V}}{60 \Omega} = 0.6 \text{ A}$$


$$I_3 = \frac{\Delta V_{4,5}}{R_{4,5}} = \frac{36 \text{ V}}{40 \Omega} = 0.9 \text{ A}$$

Example 5 :

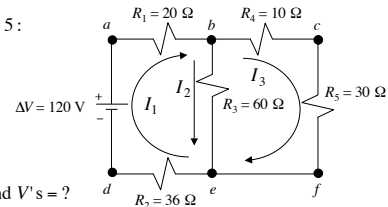

b.) I 's and V 's = ?


alternatively (Current Divider) :

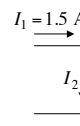

$$I_2 = I_1 \frac{R_{4,5}}{R_3 + R_{4,5}} = 1.5 \text{ A} \frac{40 \Omega}{60 \Omega + 40 \Omega} = 0.6 \text{ A}$$

$$I_3 = I_1 \frac{R_3}{R_3 + R_{4,5}} = 1.5 \text{ A} \frac{60 \Omega}{60 \Omega + 40 \Omega} = 0.9 \text{ A}$$

Example 5 :

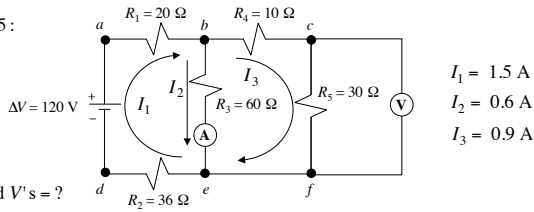

$$I_1 = 1.5 \text{ A}$$

$$I_2 = 0.6 \text{ A}$$

$$I_3 = 0.9 \text{ A}$$


b.) I 's and V 's = ?

Resistor	Current	Voltage ($\Delta V = IR$)
$R_1 = 20 \Omega$	$I_1 = 1.5 \text{ A}$	$\Delta V_1 = 30 \text{ V}$
$R_2 = 36 \Omega$	$I_1 = 1.5 \text{ A}$	$\Delta V_2 = 54 \text{ V}$
$R_3 = 60 \Omega$	$I_2 = 0.6 \text{ A}$	$\Delta V_3 = 36 \text{ V}$
$R_4 = 10 \Omega$	$I_3 = 0.9 \text{ A}$	$\Delta V_4 = 9 \text{ V}$
$R_5 = 30 \Omega$	$I_3 = 0.9 \text{ A}$	$\Delta V_5 = 27 \text{ V}$

c.) Meter readings?

Ammeter reads current $I_2 = 0.6 \text{ A}$
 Voltmeter reads voltage $\Delta V_5 = 27 \text{ V}$

Example 5 :

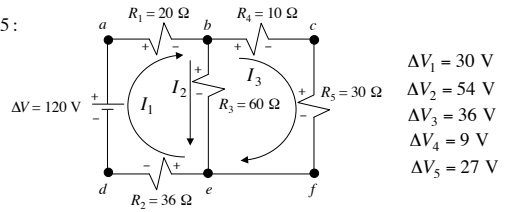

$$\Delta V_1 = 30 \text{ V}$$

$$\Delta V_2 = 54 \text{ V}$$

$$\Delta V_3 = 36 \text{ V}$$

$$\Delta V_4 = 9 \text{ V}$$

$$\Delta V_5 = 27 \text{ V}$$

d.) $V_{ae} = ?$ and $V_{fb} = ?$

$$V_{ae} = V_a - V_e$$

$$V_{fb} = V_f - V_b$$

Using point e as a reference ($V_e = 0$)

Using point b as a reference ($V_b = 0$)

$$V_d = V_e - \Delta V_2 = 0 - 54 \text{ V} = -54 \text{ V}$$

$$V_e = V_b - \Delta V_3 = 0 - 36 \text{ V} = -36 \text{ V}$$

$$V_a = V_d + \Delta V = -54 \text{ V} + 120 \text{ V} = 66 \text{ V}$$

$$V_f = V_e - \Delta V_5 = -36 \text{ V}$$

$$V_{ae} = V_a - V_e = 66 \text{ V} - 0$$


$$V_{fb} = V_f - V_b = -36 \text{ V} - 0$$

$$\boxed{V_{ae} = 66 \text{ V}}$$

$$\boxed{V_{fb} = -36 \text{ V}}$$

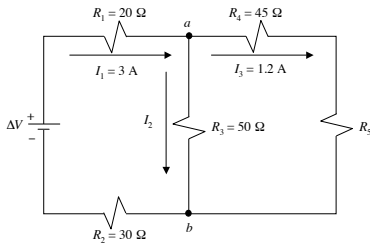Example 6:


Find the current I_2 , the resistance R_5 , and the voltage ΔV .



Electricity and Circuits

15

Example 6 :

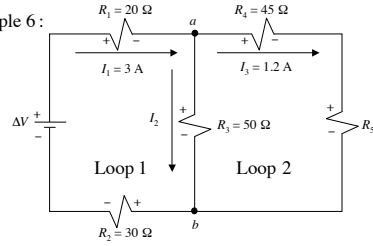

$$I_2 = ?$$

@ junction a :

$$I_1 = I_2 + I_3$$

$$I_2 = I_1 - I_3$$

$$I_2 = 3 \text{ A} - 1.2 \text{ A}$$

$$\boxed{I_2 = 1.8 \text{ A}}$$

$R_5 = ?$

$\Delta V = ?$

around Loop 2

around Loop 1

$$-\Delta V_4 - \Delta V_5 + \Delta V_3 = 0$$

$$\Delta V - \Delta V_1 - \Delta V_3 - \Delta V_2 = 0$$

$$-I_3 R_4 - I_3 R_5 + I_2 R_3 = 0$$

$$\Delta V = \Delta V_1 + \Delta V_3 + \Delta V_2$$

$$R_5 = \frac{-I_3 R_4 + I_2 R_3}{I_3}$$

$$\Delta V = I_1 R_1 + I_2 R_3 + I_1 R_2$$

$$R_5 = \frac{-(-1.2 \text{ A})(45 \Omega) + (1.8 \text{ A})(50 \Omega)}{1.2 \text{ A}}$$

$$\Delta V = (3 \text{ A})(20 \Omega) + (1.8 \text{ A})(50 \Omega) + (3 \text{ A})(30 \Omega)$$


$$\boxed{R_5 = 30 \Omega}$$

$$\boxed{\Delta V = 240 \text{ V}}$$

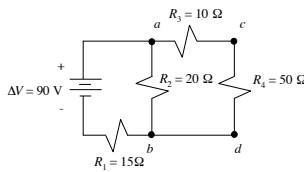Example 7:

For the circuit shown above:


- Find the equivalent resistance.
- The current and voltage for each resistor.
- The power dissipated in the circuit.
- The voltages V_{ad} and V_{bc} .






Electricity and Circuits

17

Example 7 :

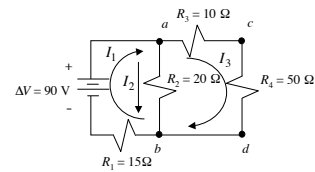

a.) $R_{eq} = ?$

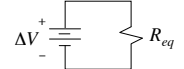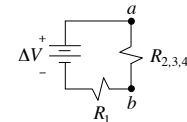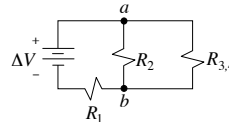

$$R_{eq} = R_1 + R_{2,3,4}$$

$$R_{eq} = 15 \Omega + 15 \Omega$$

$$\boxed{R_{eq} = 30 \Omega}$$

$$R_{3,4} = R_3 + R_4$$


$$R_{3,4} = 10 \Omega + 50 \Omega$$

$$R_{3,4} = 60 \Omega$$


$$R_{2,3,4} = \left(\frac{1}{R_2} + \frac{1}{R_{3,4}} \right)^{-1}$$

$$R_{2,3,4} = \left(\frac{1}{20 \Omega} + \frac{1}{60 \Omega} \right)^{-1} = 15 \Omega$$


Example 7 :

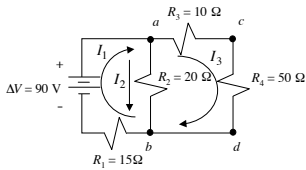

b.) I 's and V 's = ?

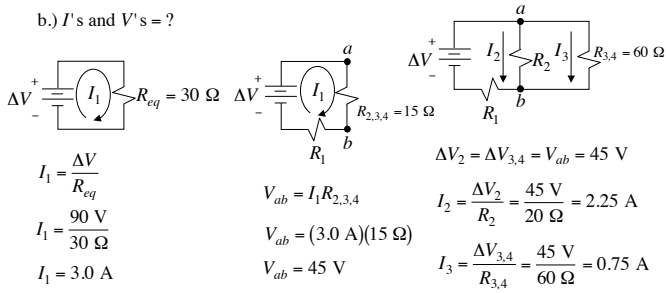

Example 7 :

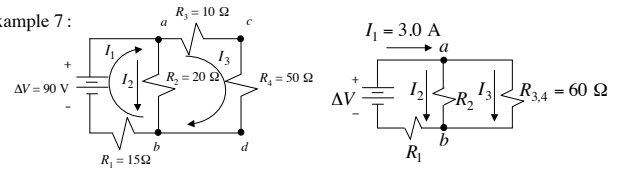


b.) I 's and V 's = ? alternatively (Current Divider) :

$$I_2 = I_1 \frac{R_{3,4}}{R_2 + R_{3,4}} = 3.0 \text{ A} \frac{60 \Omega}{20 \Omega + 60 \Omega} = 2.25 \text{ A}$$

$$I_3 = I_1 \frac{R_2}{R_2 + R_{3,4}} = 3.0 \text{ A} \frac{20 \Omega}{20 \Omega + 60 \Omega} = 0.75 \text{ A}$$

Resistor	Current	Voltage ($\Delta V = IR$)
$R_1 = 15 \Omega$	$I_1 = 3.0 \text{ A}$	$\Delta V_1 = 45 \text{ V}$
$R_2 = 20 \Omega$	$I_2 = 2.25 \text{ A}$	$\Delta V_2 = 45 \text{ V}$
$R_3 = 10 \Omega$	$I_3 = 0.75 \text{ A}$	$\Delta V_3 = 7.5 \text{ V}$
$R_4 = 60 \Omega$	$I_3 = 0.75 \text{ A}$	$\Delta V_4 = 37.5 \text{ V}$

Example 7 :

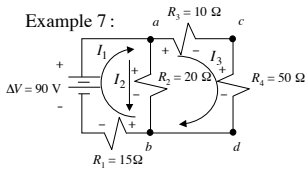

Resistor	Current	Voltage
$R_1 = 15 \Omega$	$I_1 = 3.0 \text{ A}$	$\Delta V_1 = 45 \text{ V}$
$R_2 = 20 \Omega$	$I_2 = 2.25 \text{ A}$	$\Delta V_2 = 45 \text{ V}$
$R_3 = 10 \Omega$	$I_3 = 0.75 \text{ A}$	$\Delta V_3 = 7.5 \text{ V}$
$R_4 = 60 \Omega$	$I_3 = 0.75 \text{ A}$	$\Delta V_4 = 37.5 \text{ V}$

c.) $P = ?$

$$P = \Delta V I_1 = (90 \text{ V})(3.0 \text{ A})$$

$$\boxed{P = 270 \text{ W}}$$

d.) $V_{ad} = ?$ and $V_{bc} = ?$

$$V_{ad} = V_a - V_d$$

Using point d as a reference ($V_d = 0$)

$$V_b = V_d = 0$$

$$V_a = V_b + \Delta V_2 = 0 + 45 \text{ V} = 45 \text{ V}$$

$$V_{ad} = V_a - V_d = 45 \text{ V} - 0$$

$$\boxed{V_{ad} = 45 \text{ V}}$$

$$V_{bc} = V_b - V_c$$

Using point c as a reference ($V_c = 0$)

$$V_d = V_c - \Delta V_4 = 0 - 37.5 \text{ V} = -37.5 \text{ V}$$

$$V_b = V_d = -37.5 \text{ V}$$

$$V_{bc} = V_b - V_c = -37.5 \text{ V}$$

$$\boxed{V_{bc} = -37.5 \text{ V}}$$