

### Example 1

An 18-gauge copper wire has a nominal diameter of 1.02 mm. This wire carries a constant current of 1.67 A to a 200 W lamp. The density of free electrons is  $8.5 \times 10^{28}$  electrons per cubic meter. Find the magnitude of

- the current density
- the drift velocity

Example 1:  $D = 1.2$  mm,  $I = 1.67$  A, and  $N = 8.5 \times 10^{28} \frac{\text{electrons}}{\text{m}^3}$

a.)  $J = ?$

$$J = \frac{I}{A} = \frac{I}{\pi r^2} = \frac{1.67 \text{ A}}{\pi(0.51 \times 10^{-3} \text{ m})^2}$$

$$J = 2.04 \times 10^6 \frac{\text{A}}{\text{m}^2}$$

b.)  $v_d = ?$

$$I = Nev_d A$$

$$\frac{I}{A} = Nev_d = J \text{ so } v_d = \frac{J}{Ne}$$

$$v_d = \frac{2.04 \times 10^6 \frac{\text{A}}{\text{m}^2}}{\left(8.5 \times 10^{28} \frac{\text{electrons}}{\text{m}^3}\right) \left(1.6 \times 10^{-19} \frac{\text{C}}{\text{electron}}\right)}$$

$$v_d = 1.5 \times 10^{-4} \frac{\text{m}}{\text{s}}$$

### Example 2

A 50 m long copper wire ( $\rho = 1.72 \times 10^{-8} \Omega \cdot \text{m}$ ) has a diameter of 1.0 mm and is connected to a 6 V battery with an internal resistance of 0.5  $\Omega$ . Find:

- the resistance of the wire.
- the current through the wire.
- the terminal voltage of the battery.

Example 2:


$\ell = 50$  m,  $D = 1.0$  mm,  $\mathcal{E} = 6$  V,  $\rho = 1.72 \times 10^{-8} \Omega \cdot \text{m}$ , and  $r = 0.5$   $\Omega$

a.)  $R = ?$

$$R = \frac{\rho \ell}{A} = \frac{\rho \ell}{\pi r^2} = \frac{(1.72 \times 10^{-8} \Omega \cdot \text{m})(50 \text{ m})}{\pi(0.5 \times 10^{-3} \text{ m})^2}$$

$$R = 1.1 \Omega$$

b.)  $I = ?$

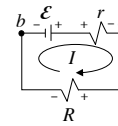

$$\mathcal{E} = Ir + IR = I(r + R)$$


$$I = \frac{\mathcal{E}}{r + R} = \frac{6 \text{ V}}{0.5 \Omega + 1.1 \Omega}$$

$$I = 3.75 \text{ A}$$

c.)  $V_{ab} = ?$

$$V_{ab} = \mathcal{E} - Ir = 6 \text{ V} - (3.75 \text{ A})(0.5 \Omega)$$

$$V_{ab} = 4.125 \text{ V}$$

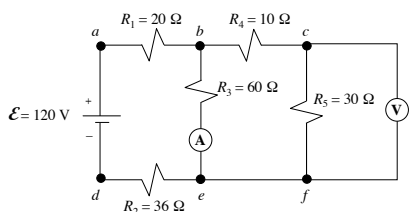


### Example 3


For the circuit shown above:

- Find the equivalent resistance.
- The current and voltage for each resistor.
- The readings on the ammeter and on the voltmeter.
- The voltages  $V_{ae}$  and  $V_{db}$ .

Example 3:

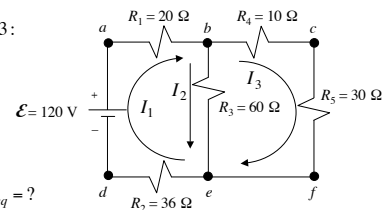


a.)  $R_{eq} = ?$

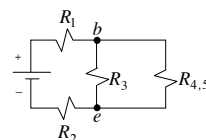

$$R_{4,5} = R_4 + R_5$$


$$R_{4,5} = 10 \Omega + 30 \Omega$$

$$R_{4,5} = 40 \Omega$$

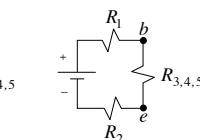

$$R_{3,4,5} = \left( \frac{1}{R_3} + \frac{1}{R_{4,5}} \right)^{-1}$$
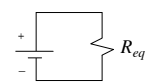
$$R_{3,4,5} = \left( \frac{1}{60 \Omega} + \frac{1}{40 \Omega} \right)^{-1} = 24 \Omega$$




$$R_{eq} = R_1 + R_2 + R_{3,4,5}$$


$$R_{eq} = 20 \Omega + 36 \Omega + 24 \Omega$$

$$R_{eq} = 80 \Omega$$


Example 3:

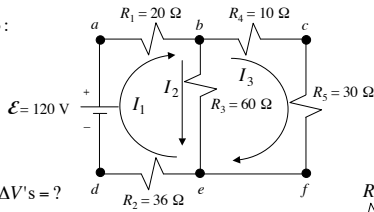

b.)  $I$ 's and  $\Delta V$ 's = ?

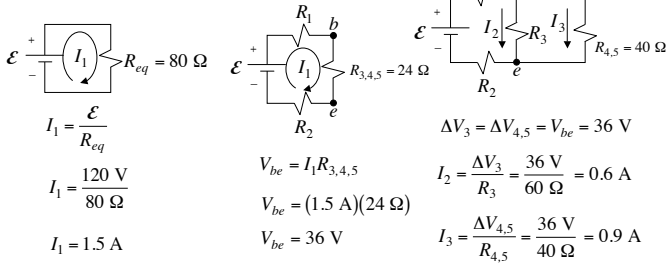


Example 3:

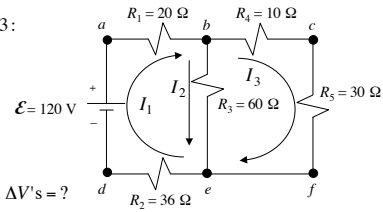


b.)  $I$ 's and  $\Delta V$ 's = ?

alternatively (Current Divider):

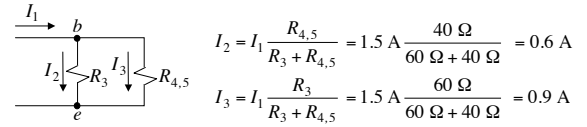

Example 3:

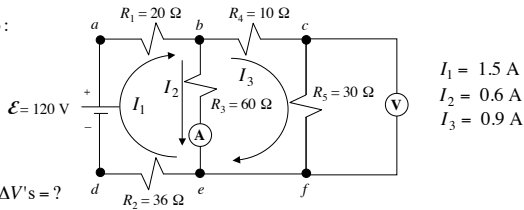


b.)  $I$ 's and  $\Delta V$ 's = ?

Resistor	Current	Voltage ( $\Delta V = IR$ )
$R_1 = 20 \Omega$	$I_1 = 1.5 \text{ A}$	$\Delta V_1 = 30 \text{ V}$
$R_2 = 36 \Omega$	$I_1 = 1.5 \text{ A}$	$\Delta V_2 = 54 \text{ V}$
$R_3 = 60 \Omega$	$I_2 = 0.6 \text{ A}$	$\Delta V_3 = 36 \text{ V}$
$R_4 = 10 \Omega$	$I_3 = 0.9 \text{ A}$	$\Delta V_4 = 9 \text{ V}$
$R_5 = 30 \Omega$	$I_3 = 0.9 \text{ A}$	$\Delta V_5 = 27 \text{ V}$

c.) Meter readings?

Ammeter reads current  $I_2 = 0.6 \text{ A}$   
 Voltmeter reads voltage  $V_5 = 27 \text{ V}$

Example 3:

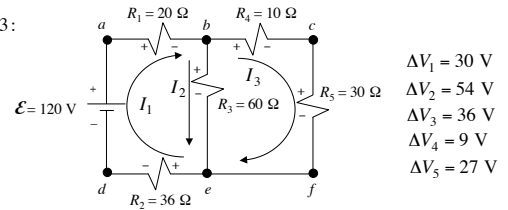

d.)  $V_{ae} = ?$  and  $V_{db} = ?$

$$V_{ae} = V_a - V_e$$

$$V_{db} = V_d - V_b$$

Using point  $e$  as a reference ( $V_e = 0$ )      Using point  $b$  as a reference ( $V_b = 0$ )

$$V_d = V_e - \Delta V_2 = 0 - 54 \text{ V} = -54 \text{ V}$$


$$V_e = V_b - \Delta V_3 = 0 - 36 \text{ V} = -36 \text{ V}$$

$$V_a = V_d + \mathcal{E} = -54 \text{ V} + 120 \text{ V} = 66 \text{ V}$$

$$V_d = V_e - \Delta V_2 = -36 \text{ V} - 54 \text{ V} = -90 \text{ V}$$

$$V_{ae} = V_a - V_e = 66 \text{ V} - 0 = 66 \text{ V}$$
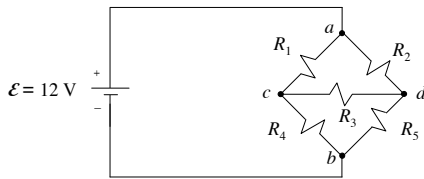
$$V_{db} = V_d - V_b = -90 \text{ V} - 0 = -90 \text{ V}$$




$\mathcal{E} = 12 \text{ V}$

Example 4

In the circuit shown above:  $R_1 = 6 \Omega$ ,  $R_2 = 3 \Omega$ ,  $R_4 = R_5 = 4 \Omega$ , and  $R_3 = 2 \Omega$ .

- Find the equivalent resistance.
- The current and voltage for each resistor.
- Suppose  $R_5$  is variable and can have any resistance. What value will result in no current passing through  $R_3$ ?

Example 4:

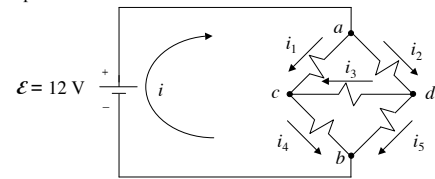

Loop Rule Equations

$$\mathcal{E} = i_1 R_1 + i_4 R_4$$

$$0 = -i_1 R_1 + i_2 R_2 + i_3 R_3$$

$$0 = -i_3 R_3 - i_4 R_4 + i_5 R_5$$

Junction Rule Equations

$$i = i_1 + i_2 \text{ at } a$$

$$i_2 = i_3 + i_5 \text{ at } d$$

$$i_1 + i_3 = i_4 \text{ at } c$$

Example 4 :

$$\begin{aligned} \mathcal{E} &= i_1 R_1 + i_4 R_4 & i &= i_1 + i_2 \text{ at } a \\ 0 &= -i_1 R_1 + i_2 R_2 + i_3 R_3 & i_2 &= i_3 + i_5 \text{ at } d \\ 0 &= -i_3 R_3 - i_4 R_4 + i_5 R_5 & i_1 + i_3 &= i_4 \text{ at } c \end{aligned}$$

$$\begin{pmatrix} 0 & R_1 & 0 & 0 & R_4 & 0 \\ 0 & -R_1 & R_2 & R_3 & 0 & 0 \\ 0 & 0 & 0 & -R_3 & -R_4 & R_5 \\ -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & -1 & 0 & -1 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{pmatrix} = \begin{pmatrix} \mathcal{E} \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$


Example 4 :

$$\begin{pmatrix} 0 & 6 & 0 & 0 & 4 & 0 \\ 0 & -6 & 3 & 2 & 0 & 0 \\ 0 & 0 & 0 & -2 & -4 & 4 \\ -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & -1 & 0 & -1 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{pmatrix} = \begin{pmatrix} 12 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

$$\begin{pmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{pmatrix} = \begin{pmatrix} 2.97 \text{ A} \\ 1.06 \text{ A} \\ 1.91 \text{ A} \\ 1.40 \text{ A} \\ 1.57 \text{ A} \end{pmatrix}$$

Example 4 :

### Loop Method

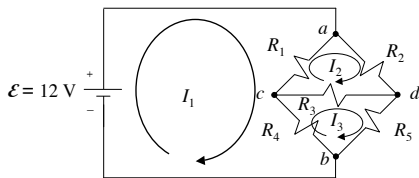

Loop Equations

$$\begin{aligned} \mathcal{E} &= (R_1 + R_4)I_1 - R_1 I_2 - R_4 I_3 \\ 0 &= -R_1 I_1 + (R_1 + R_2 + R_3)I_2 - R_3 I_3 \\ 0 &= -R_4 I_1 - R_3 I_2 + (R_3 + R_4 + R_5)I_3 \end{aligned}$$

Example 4 :

### Loop Method

$$\begin{aligned} \mathcal{E} &= (R_1 + R_4)I_1 - R_1 I_2 - R_4 I_3 \\ 0 &= -R_1 I_1 + (R_1 + R_2 + R_3)I_2 - R_3 I_3 \\ 0 &= -R_4 I_1 - R_3 I_2 + (R_3 + R_4 + R_5)I_3 \end{aligned}$$

$$\begin{pmatrix} R_1 + R_4 & -R_1 & -R_4 \\ -R_1 & R_1 + R_2 + R_3 & -R_3 \\ -R_4 & -R_3 & R_3 + R_4 + R_5 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} \mathcal{E} \\ 0 \\ 0 \end{pmatrix}$$

$$\begin{pmatrix} 10 \Omega & -6 \Omega & -4 \Omega \\ -6 \Omega & 11 \Omega & -2 \Omega \\ -4 \Omega & -2 \Omega & 10 \Omega \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 12 \text{ V} \\ 0 \\ 0 \end{pmatrix}$$


$$\begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 2.97 \text{ A} \\ 1.91 \text{ A} \\ 1.57 \text{ A} \end{pmatrix}$$

Example 4 :

a.)  $R_{eq} = ?$   
 $R_{eq} = \frac{\mathcal{E}}{I_1} = \frac{12 \text{ V}}{2.97 \text{ A}} = 4.04 \Omega$

b.)  $I$ 's and  $\Delta V$ 's = ?

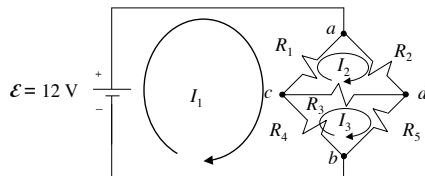
$$\begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 2.97 \text{ A} \\ 1.91 \text{ A} \\ 1.57 \text{ A} \end{pmatrix}$$



Resistor	Current	Voltage
$R_1 = 6 \Omega$	$i_1 = I_1 - I_2 = 1.06 \text{ A}$	$\Delta V_1 = 6.36 \text{ V}$
$R_2 = 3 \Omega$	$i_2 = I_2 = 1.91 \text{ A}$	$\Delta V_2 = 5.73 \text{ V}$
$R_3 = 2 \Omega$	$i_3 = I_2 - I_3 = 0.34 \text{ A}$	$\Delta V_3 = 0.68 \text{ V}$
$R_4 = 4 \Omega$	$i_4 = I_1 - I_3 = 1.4 \text{ A}$	$\Delta V_4 = 5.6 \text{ V}$
$R_5 = 4 \Omega$	$i_5 = I_3 = 1.57 \text{ A}$	$\Delta V_5 = 6.28 \text{ V}$

Example 4 :

c.)  $R_5 = ?$  such that  $i_3 = 0$

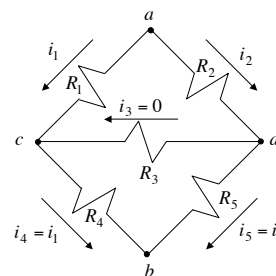

$$\begin{aligned} R_1 &= 6 \Omega \\ R_2 &= 3 \Omega \\ R_3 &= 2 \Omega \\ R_4 &= 4 \Omega \\ R_5 &= ? \end{aligned}$$

$$V_c = V_d$$

$$V_{ac} = V_{ad}$$

$$i_1 R_1 = i_2 R_2$$

$$i_1 = i_2 \frac{R_2}{R_1}$$

$$V_{cb} = V_{db}$$


$$i_4 R_4 = i_5 R_5$$

$$i_4 R_4 = i_2 R_5$$

$$i_2 \frac{R_2}{R_1} R_4 = i_2 R_5$$

$$R_5 = \frac{R_2 R_4}{R_1} = \frac{(3 \Omega)(4 \Omega)}{6 \Omega}$$

$$R_5 = 2 \Omega$$

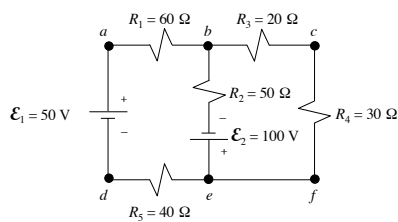

### Example 5


For the circuit shown above:

- Find the current in each battery.
- The amount of energy dissipated in the circuit in 15 minutes.
- The voltages  $V_{ae}$  and  $V_{fb}$ .

Direct Current Circuits

19

### Example 5 :

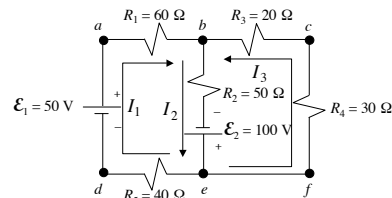

- a.)  $I_1 = ?$  and  $I_2 = ?$

@ junction b : (1)  $I_1 + I_3 = I_2$

around loop abed : (2)  $\mathcal{E}_1 + \mathcal{E}_2 = I_1(R_1 + R_5) + I_2R_2$

around loop bcfe : (3)  $\mathcal{E}_2 = I_2R_2 + I_3(R_3 + R_4)$

(1 and 2)  $\mathcal{E}_1 + \mathcal{E}_2 = I_1(R_1 + R_5) + (I_1 + I_3)R_2 = I_1(R_1 + R_2 + R_5) + I_3R_2$

$150 \text{ V} = I_1(150 \Omega) + I_3(50 \Omega)$

(1 and 3)  $\mathcal{E}_2 = (I_1 + I_3)R_2 + I_3(R_3 + R_4) = I_1R_2 + I_3(R_2 + R_3 + R_4)$

$100 \text{ V} = I_1(50 \Omega) + I_3(100 \Omega)$

### Example 5 :

- a.)  $I_1 = ?$  and  $I_2 = ?$

$(150 \text{ V} = I_1(150 \Omega) + I_3(50 \Omega))2 \quad 300 \text{ V} = I_1(300 \Omega) + I_3(100 \Omega)$

$300 \text{ V} = I_1(300 \Omega) + I_3(100 \Omega)$

$-(100 \text{ V} = I_1(50 \Omega) + I_3(100 \Omega))$

$200 \text{ V} = I_1(250 \Omega)$

$I_1 = \frac{200 \text{ V}}{250 \Omega}$

$I_1 = 0.8 \text{ A}$

$I_3 = \frac{300 \text{ V} - I_1(300 \Omega)}{100 \Omega}$

$I_3 = \frac{300 \text{ V} - (0.8 \text{ A})(300 \Omega)}{100 \Omega}$

$I_3 = 0.6 \text{ A}$

$I_2 = I_1 + I_3 = 0.8 \text{ A} + 0.6 \text{ A}$

$I_2 = 1.4 \text{ A}$

- b.)  $t = 15 \text{ min}$ ,  $E = ?$


$E = Pt = (P_1 + P_2)t$

$E = (\mathcal{E}_1 I_1 + \mathcal{E}_2 I_2)t$

$E = ((50 \text{ V})(0.8 \text{ A}) + (100 \text{ V})(1.4 \text{ A}))(3000 \text{ s})$

$E = 162,000 \text{ J}$

### Example 5 :

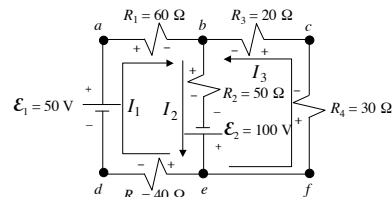

- c.)  $V_{ae} = ?$  and  $V_{fb} = ?$

$V_{ae} = V_a - V_e$

$V_{fb} = V_f - V_b$

Using point e as a reference ( $V_e = 0$ )

Using point b as a reference ( $V_b = 0$ )

$V_a = V_e - \Delta V_5 + \mathcal{E}_1 = V_e - I_1 R_5 + \mathcal{E}_1$

$V_f = V_b + \Delta V_3 + \Delta V_4 = V_b + I_3 R_3 + I_3 R_4$

$V_a = 0 - (0.8 \text{ A})(40 \Omega) + 50 \text{ V}$

$V_f = 0 + (0.6 \text{ A})(20 \Omega) + (0.6 \text{ A})(30 \Omega)$

$V_a = 18 \text{ V}$


$V_f = 30 \text{ V}$

$V_{ae} = V_a - V_e = 18 \text{ V} - 0$

$V_{fb} = V_f - V_b = 30 \text{ V} - 0$

$V_{ae} = 18 \text{ V}$

$V_{fb} = 30 \text{ V}$

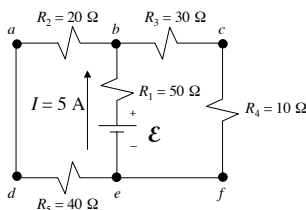

### Example 6


For the circuit shown above:

- Find the current through each resistor.
- Find the emf  $\mathcal{E}$  of the battery.

Direct Current Circuits

23

### Example 6 :

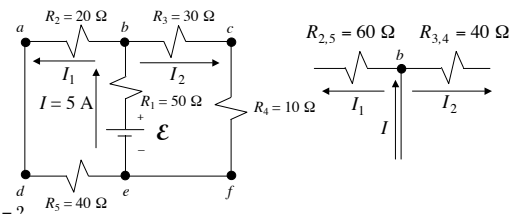

- a.)  $I_1 = ?$  and  $I_2 = ?$

@ junction b : (current divider)

$I_1 = I \frac{R_{3,4}}{R_{2,5} + R_{3,4}} = 5 \text{ A} \frac{40 \Omega}{60 \Omega + 40 \Omega}$

$I_2 = I \frac{R_{2,5}}{R_{2,5} + R_{3,4}} = 5 \text{ A} \frac{60 \Omega}{60 \Omega + 40 \Omega}$

$I_1 = 2 \text{ A}$

$I_2 = 3 \text{ A}$

- b.)  $\mathcal{E} = ?$

around loop ebad :  $\mathcal{E} = IR_1 + I_1(R_2 + R_5)$

around loop ebcf :  $\mathcal{E} = IR_1 + I_2(R_3 + R_4)$


$\mathcal{E} = (5 \text{ A})(50 \Omega) + (2 \text{ A})(20 \Omega + 40 \Omega)$

$\mathcal{E} = (5 \text{ A})(50 \Omega) + (3 \text{ A})(30 \Omega + 10 \Omega)$

$\mathcal{E} = 370 \text{ V}$

$\mathcal{E} = 370 \text{ V}$



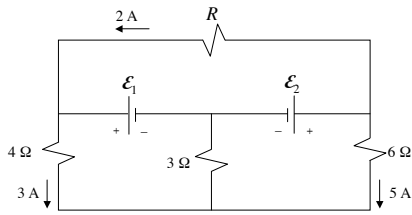


### Example 7

In the circuit shown above find

- the current in the  $3 \Omega$  resistor
- the unknown emf's  $\mathcal{E}_1$  and  $\mathcal{E}_2$
- the resistance  $R$

### Example 7:

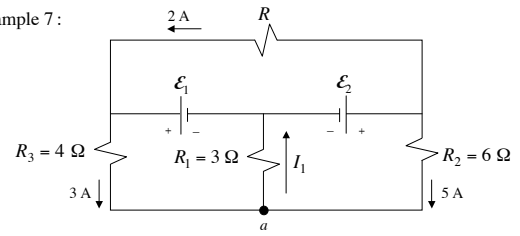

- current in  $R_1 = ?$   
@ junction  $a$ :  $I_1 = 3 \text{ A} + 5 \text{ A}$   
 $I_1 = 8 \text{ A}$
- $\mathcal{E}_1 = ?$  and  $\mathcal{E}_2 = ?$   
 $\mathcal{E}_1 = \Delta V_3 + \Delta V_1 = (3 \text{ A})(4 \Omega) + (8 \text{ A})(3 \Omega)$   
 $\mathcal{E}_1 = 36 \text{ V}$   
 $\mathcal{E}_2 = \Delta V_2 + \Delta V_1 = (5 \text{ A})(6 \Omega) + (8 \text{ A})(3 \Omega)$   
 $\mathcal{E}_2 = 54 \text{ V}$
- $R = ?$   
 $\Delta V_R = \mathcal{E}_2 - \mathcal{E}_1$   
 $I_R R = \mathcal{E}_2 - \mathcal{E}_1$   
 $R = \frac{\mathcal{E}_2 - \mathcal{E}_1}{I_R} = \frac{54 \text{ V} - 36 \text{ V}}{2 \text{ A}}$   
 $R = 9 \Omega$

### Example 8


A galvanometer has a coil resistance of  $500 \Omega$  and a full scale current of  $10 \mu\text{A}$ . Show how to make

- A voltmeter with a full scale reading of  $5 \text{ V}$ .
- An ammeter with a full scale reading of  $5 \text{ mA}$ .

### Example 8:

$$R_C = 500 \Omega \text{ and } I_{fs} = 10 \mu\text{A}$$

- $5 \text{ V}$  full scale voltmeter

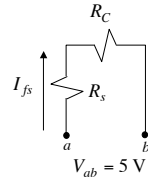

$$V_{ab} = \Delta V_{R_g} + \Delta V_{R_C}$$


$$V_{ab} = I_{fs} R_g + I_{fs} R_C$$

$$R_s = \frac{V_{ab}}{I_{fs}} - R_C$$

$$R_s = \frac{5 \text{ V}}{10 \times 10^{-6} \text{ A}} - 500 \Omega$$

$$R_s = 499,500 \Omega$$

- $5 \text{ mA}$  full scale ammeter

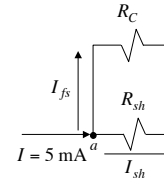

$$V_{ab} = \Delta V_{R_{sh}} = \Delta V_{R_C}$$


$$I_{sh} R_{sh} = I_{fs} R_C$$

$$(I - I_{fs}) R_{sh} = I_{fs} R_C$$

$$R_{sh} = \frac{I_{fs} R_C}{(I - I_{fs})} = \frac{(10 \times 10^{-6} \text{ A})(500 \Omega)}{(5 \times 10^{-3} \text{ A} - 10 \times 10^{-6} \text{ A})}$$

$$R_{sh} = 1,002 \Omega$$

### Example 9:

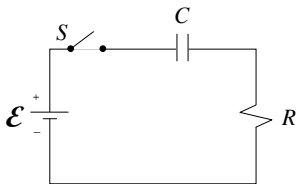


An ideal battery with an emf  $\mathcal{E} = 100 \text{ V}$  is connected to a resistor with resistance  $R = 100 \Omega$  and an initially uncharged capacitor with capacitance  $C = 1 \mu\text{F}$ . The circuit is completed when switch  $S$  is closed at time  $t = 0$ .


- Find the current through and voltage across each device immediately after the switch is closed.
- A long time after the switch is closed, find the charge on the capacitor and the voltage across the resistor.
- What is the charge on the capacitor after  $0.2 \text{ ms}$ ?
- Find the total energy dissipated in the resistor.
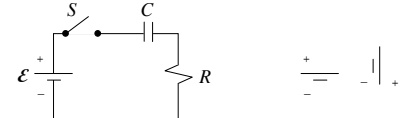
### Example 9:

$$\mathcal{E} = 100 \text{ V}, R = 100 \Omega, \text{ and } C = 1 \mu\text{F}$$



- $\Delta V$ 's and  $I$ 's @  $t = 0$

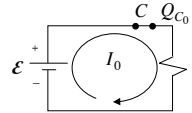

$$\mathcal{E} = I_0 R$$


$$I_0 = \frac{\mathcal{E}}{R} = \frac{100 \text{ V}}{100 \Omega} = 1 \text{ A}$$

$$I_{R_0} = I_{C_0} = 1 \text{ A}$$

$$\Delta V_{R_0} = 100 \text{ V}$$

$$\Delta V_{C_0} = 0$$

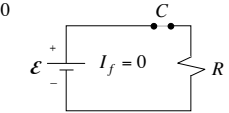- $\Delta V_R$  and  $Q_C$  @  $t = \infty$



$$\Delta V_{R_f} = I_f R$$

$$\Delta V_{R_f} = 0$$

$$\Delta V_{C_f} = \mathcal{E}$$


$$\Delta V_{C_f} = 100 \text{ V}$$

$$Q_{C_f} = C \Delta V_{C_f} = (1 \times 10^{-6} \text{ F})(100 \text{ V})$$

$$Q_{C_f} = 100 \mu\text{C}$$

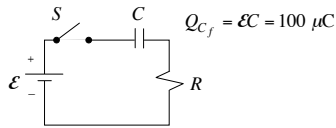Example 9

$\mathcal{E} = 100 \text{ V}$ ,  $R = 100 \ \Omega$ , and  $C = 1 \ \mu\text{F}$



c.)  $q_C$  @  $t = 0.2 \text{ ms}$

$$q_C = Q_{C_f} (1 - e^{-t/\tau})$$

$$\tau = RC = (100 \ \Omega)(1 \times 10^{-6} \text{ F})$$

$$\tau = 0.1 \text{ ms}$$

$$q_C = (100 \ \mu\text{C})(1 - e^{-(0.2 \text{ ms}/0.1 \text{ ms})})$$

$q_C = 86.5 \ \mu\text{C}$

d.)  $E_R$  from  $t = 0$  to  $\infty$

$$P = \frac{dE}{dt} \text{ so } E = \int P dt$$

$$P = i^2 R$$

$$q_C = Q_{C_f} (1 - e^{-t/\tau}) = \mathcal{E}C (1 - e^{-t/\tau})$$

$$i = \frac{dq}{dt} = \frac{d}{dt} (\mathcal{E}C (1 - e^{-t/\tau}))$$

$$i = -\mathcal{E}C e^{-t/\tau} \left( \frac{-1}{RC} \right)$$

$$i = \frac{\mathcal{E}}{R} e^{-t/\tau} = I_0 e^{-t/\tau}$$

Example 9 :

d.)  $E_R$  from  $t = 0$  to  $\infty$

$$E = \int P dt = \int_0^\infty i^2 R dt$$

$$E = \int_0^\infty \left( \frac{\mathcal{E}}{R} e^{-t/\tau} \right)^2 R dt$$

$$E = \int_0^\infty \frac{\mathcal{E}^2}{R} e^{-2t/\tau} R dt = \int_0^\infty \frac{\mathcal{E}^2}{R} e^{-2t/\tau} R dt$$


$$E = \frac{-\mathcal{E}^2 C}{2} \int_0^\infty e^{-2t/\tau} \left( \frac{-2}{RC} \right) dt$$

$$E = \frac{-\mathcal{E}^2 C}{2} e^{-2t/\tau} \Big|_0^\infty = \frac{-\mathcal{E}^2 C}{2} (e^{-\infty} - e^{-0})$$

$$E = \frac{-\mathcal{E}^2 C}{2} (0 - 1) = \frac{\mathcal{E}^2 C}{2} = \frac{1}{2} C \mathcal{E}^2$$

$$E = \frac{1}{2} (1 \times 10^{-6} \text{ F})(100 \text{ V})^2$$

$E = 5 \text{ mJ}$

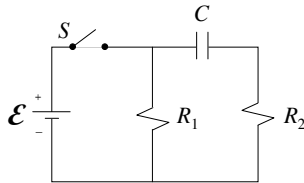

Example 10:


An ideal battery with an emf  $\mathcal{E} = 12 \text{ V}$ , two resistors with resistances  $R_1 = 4 \ \Omega$  and  $R_2 = 6 \ \Omega$ , and an initially uncharged capacitor with capacitance  $C = 6 \ \mu\text{F}$ . The circuit is completed when switch  $S$  is closed at time  $t = 0$ .

- a.) At time  $t = 2\tau$ , what is the potential difference across the capacitor?  
 b.) At time  $t = 2\tau$ , what are the potential differences across the two resistors? Do those potential differences increase, decrease, or remain the same while the capacitor is being charged?


Direct Current Circuits

33

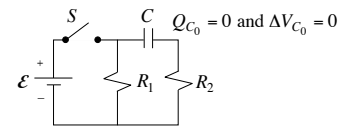Example 10:  $\mathcal{E} = 12 \text{ V}$ ,  $R_1 = 4 \ \Omega$ ,  $R_2 = 6 \ \Omega$ , and  $C = 6 \ \mu\text{F}$



a.) @  $t = 2\tau$ ,  $\Delta v_C = ?$

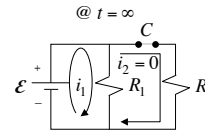

$$i_1 = \frac{\mathcal{E}}{R_1} = \frac{12 \text{ V}}{4 \ \Omega} = 3 \text{ A}$$

$$\Delta v_{R_1} = i_1 R_1 = (3 \text{ A})(4 \ \Omega) = 12 \text{ V}$$


$$\Delta v_{R_1} = \Delta v_{C_f} = 12 \text{ V}$$

$$\Delta v_C(t) = \Delta v_{C_f} (1 - e^{-t/\tau})$$

$$\Delta v_C(2\tau) = (12 \text{ V})(1 - e^{-2})$$


$\Delta v_C(2\tau) = 10.38 \text{ V}$

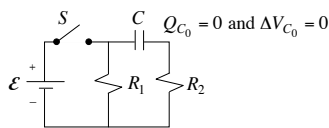Example 10:  $\mathcal{E} = 12 \text{ V}$ ,  $R_1 = 4 \ \Omega$ ,  $R_2 = 6 \ \Omega$ , and  $C = 6 \ \mu\text{F}$



b.) @  $t = 2\tau$ ,  $\Delta v_{R_1} = ?$  and  $\Delta v_{R_2} = ?$

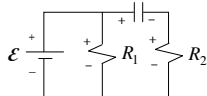@  $t = 2\tau$   $\Delta v_C = 10.38 \text{ V}$



$\Delta v_{R_1} = \mathcal{E} = 12 \text{ V}$

$$\Delta v_{R_1} - \Delta v_C - \Delta v_{R_2} = 0$$

$$\Delta v_{R_2} = \Delta v_{R_1} - \Delta v_C$$

$$\Delta v_{R_2} = 12 \text{ V} - 10.38 \text{ V}$$

$\Delta v_{R_2} = 1.62 \text{ V}$

$\Delta v_{R_1}$  is always  $12 \text{ V}$


$\Delta v_{R_2}$  is decreasing

Example 10: (continued)

c.) A long time after the switch has been closed the switch is opened.

i.) Write an equation for the charge on the capacitor after the switch is opened.

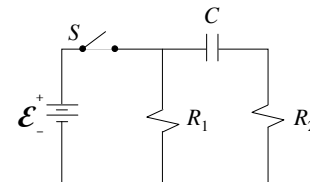
ii.) Write an equation for the voltage on each resistor after the switch is opened.



Direct Current Circuits

36

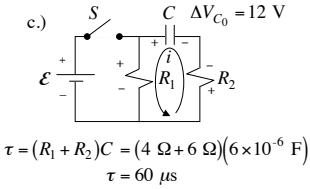Example 10:  $\mathcal{E} = 12 \text{ V}$ ,  $R_1 = 4 \text{ } \Omega$ ,  $R_2 = 6 \text{ } \Omega$ , and  $C = 6 \text{ } \mu\text{F}$



i.)  $q_C(t) = ?$   
 $q_C(t) = Q_{C_0} e^{-t/\tau}$   
 $Q_{C_0} = C \Delta V_{C_0} = (6 \times 10^{-6} \text{ F})(12 \text{ V})$   
 $Q_{C_0} = 72 \text{ } \mu\text{C}$

$q_C(t) = (72 \text{ } \mu\text{C}) e^{-t/60 \text{ } \mu\text{s}}$

ii.)  $\Delta v_{R_1}(t) = ?$  and  $\Delta v_{R_2}(t) = ?$

$i(t) = I_0 e^{-t/\tau}$   
 $I_0 = \frac{\Delta V_{C_0}}{R_1 + R_2} = \frac{12 \text{ V}}{4 \text{ } \Omega + 6 \text{ } \Omega}$   
 $I_0 = 1.2 \text{ A}$

$\Delta v_{R_1}(t) = (1.2 \text{ A})(4 \text{ } \Omega) e^{-t/60 \text{ } \mu\text{s}}$

$\Delta v_{R_1}(t) = (4.8 \text{ V}) e^{-t/60 \text{ } \mu\text{s}}$


$\Delta v_{R_2}(t) = (1.2 \text{ A})(6 \text{ } \Omega) e^{-t/60 \text{ } \mu\text{s}}$

$\Delta v_{R_2}(t) = (7.2 \text{ V}) e^{-t/60 \text{ } \mu\text{s}}$

$\Delta v_{R_1}(t) = i(t)R_1 = I_0 R_1 e^{-t/\tau}$

$\Delta v_{R_2}(t) = i(t)R_2 = I_0 R_2 e^{-t/\tau}$


Example 11:

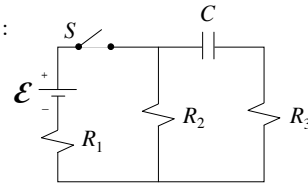

In the circuit above  $\mathcal{E} = 1000 \text{ V}$ ,  $C = 10 \text{ } \mu\text{F}$ , and  $R_1 = R_2 = R_3 = 1 \text{ M}\Omega$ . The capacitor is completely uncharged when switch  $S$  is closed.


- Determine the current through each resistor at  $t = 0$  and  $t = \infty$ .
- Draw a graph of the potential difference for each resistor for  $t = 0$  to  $t = \infty$ .

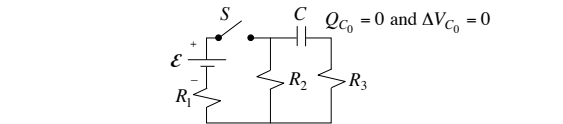Example 11:  $\mathcal{E} = 1000 \text{ V}$ ,  $R_1 = R_2 = R_3 = 1 \text{ M}\Omega$ , and  $C = 10 \text{ } \mu\text{F}$



a.)  $i$ 's @  $t = 0$  and  $t = \infty$


@  $t = 0$   $C \Delta V_{C_0} = 0$

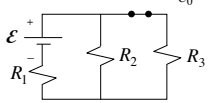

$R_{2,3} = \left( \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$

$R_{2,3} = \left( \frac{1}{1 \text{ M}\Omega} + \frac{1}{1 \text{ M}\Omega} \right)^{-1}$

$R_{2,3} = 0.5 \text{ M}\Omega$

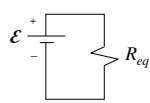


$R_{eq} = R_{2,3} + R_1$

$R_{eq} = 0.5 \text{ M}\Omega + 1 \text{ M}\Omega$


$R_{eq} = 1.5 \text{ M}\Omega$

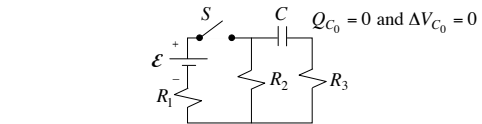Example 11:  $\mathcal{E} = 1000 \text{ V}$ ,  $R_1 = R_2 = R_3 = 1 \text{ M}\Omega$ , and  $C = 10 \text{ } \mu\text{F}$



a.)  $i$ 's @  $t = 0$  and  $t = \infty$


@  $t = 0$

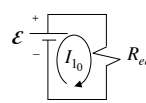

$I_{1_0} = \frac{\mathcal{E}}{R_{eq}}$

$I_{1_0} = \frac{1000 \text{ V}}{1.5 \text{ M}\Omega}$


$I_{1_0} = 0.667 \text{ mA}$

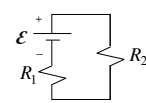

$\Delta V_{2,3} = I_{1_0} R_{2,3}$

$\Delta V_{2,3} = (0.667 \text{ mA})(0.5 \text{ M}\Omega)$

$\Delta V_{2,3} = 333.3 \text{ V}$

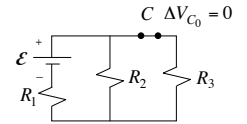

$\Delta V_2 = \Delta V_3 = \Delta V_{2,3} = 333.3 \text{ V}$


$I_{2_0} = \frac{\Delta V_2}{R_2} = \frac{333.3 \text{ V}}{1.5 \text{ M}\Omega}$

$I_{2_0} = 0.333 \text{ mA}$

$I_{3_0} = \frac{\Delta V_3}{R_3} = \frac{333.3 \text{ V}}{1.5 \text{ M}\Omega}$


$I_{3_0} = 0.333 \text{ mA}$

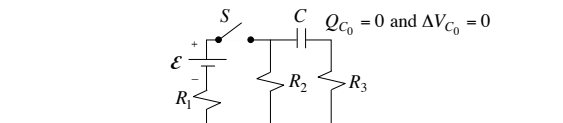Example 11:  $\mathcal{E} = 1000 \text{ V}$ ,  $R_1 = R_2 = R_3 = 1 \text{ M}\Omega$ , and  $C = 10 \text{ } \mu\text{F}$



a.)  $i$ 's @  $t = 0$  and  $t = \infty$

@  $t = \infty$   $C \Delta V_{C_0} = 0$

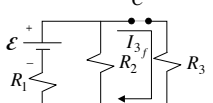

$I_{3_f} = 0$

$R_{eq} = R_1 + R_2$

$R_{eq} = 1 \text{ M}\Omega + 1 \text{ M}\Omega$

$R_{eq} = 2 \text{ M}\Omega$

$I_f = \frac{\mathcal{E}}{R_{eq}}$


$I_f = \frac{1000 \text{ V}}{2 \text{ M}\Omega} = 0.500 \text{ mA}$

$I_{1_f} = I_{2_f} = I_f$

$I_{1_f} = 0.500 \text{ mA}$

$I_{2_f} = 0.500 \text{ mA}$

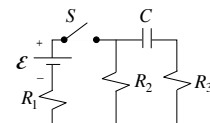Example 11:  $\mathcal{E} = 1000 \text{ V}$ ,  $R_1 = R_2 = R_3 = 1 \text{ M}\Omega$ , and  $C = 10 \text{ } \mu\text{F}$



@  $t = 0$

$I_{1_0} = 0.667 \text{ mA}$

$I_{2_0} = 0.333 \text{ mA}$

$I_{3_0} = 0.333 \text{ mA}$

@  $t = \infty$

$I_{1_f} = 0.500 \text{ mA}$


$I_{2_f} = 0.500 \text{ mA}$

$I_{3_f} = 0$


b.) graphs of voltage across each resistor for  $t = 0$  to  $t = \infty$

$\Delta V_{1_0} = I_{1_0} R_1 = (0.667 \times 10^{-3} \text{ A})(1 \times 10^6 \text{ } \Omega) = 667 \text{ V}$

$\Delta V_{1_f} = I_{1_f} R_1 = (0.500 \times 10^{-3} \text{ A})(1 \times 10^6 \text{ } \Omega) = 500 \text{ V}$

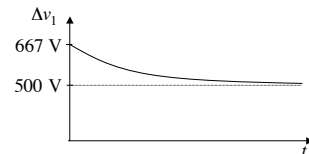

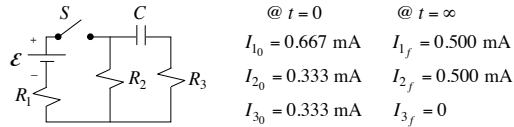
Example 11:  $\mathcal{E} = 1000 \text{ V}$ ,  $R_1 = R_2 = R_3 = 1 \text{ M}\Omega$ , and  $C = 10 \text{ }\mu\text{F}$




b.) graphs of voltage across each resistor for  $t = 0$  to  $t = \infty$

$$\Delta V_{2_0} = I_{2_0} R_2 = (0.333 \times 10^{-3} \text{ A})(1 \times 10^6 \text{ }\Omega) = 333 \text{ V}$$

$$\Delta V_{2_f} = I_{2_f} R_2 = (0.500 \times 10^{-3} \text{ A})(1 \times 10^6 \text{ }\Omega) = 500 \text{ V}$$

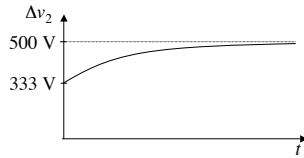

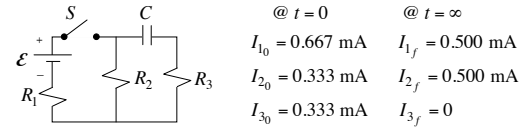Example 11:  $\mathcal{E} = 1000 \text{ V}$ ,  $R_1 = R_2 = R_3 = 1 \text{ M}\Omega$ , and  $C = 10 \text{ }\mu\text{F}$



b.) graphs of voltage across each resistor for  $t = 0$  to  $t = \infty$

$$\Delta V_{3_0} = I_{3_0} R_3 = (0.333 \times 10^{-3} \text{ A})(1 \times 10^6 \text{ }\Omega) = 333 \text{ V}$$

$$\Delta V_{3_f} = I_{3_f} R_3 = (0)(1 \times 10^6 \text{ }\Omega) = 0$$

