#### **Electric Current (Charges in Motion)**

#### Electric Current (I)

The net amount of charge that passes through a conductor per unit time at any point. Current is defined as:



Electric current is measured in *coulomb's per second* or *amperes*. (1A = 1 C/s)

In a single circuit, the current at any instant is the same at one point as any other point. (Charge is conserved.)

Direct Current Circuits

2

4

Direct Current Circuits

1

3

5

**Direct Current Circuits** 

#### Drift Velocity

The free electrons in conductors are in constant random motion, so there is no net flow of charge in any one particular direction.

If a steady electric field  $\bar{E}$  is established inside a conductor then charged particles are subjected to a steady force  $\bar{F} = q\bar{E}$ .

The charges moving in a conductor have frequent collisions with the massive nearly stationary ions of the material.

Direct Current Circuits

#### **Drift Velocity**

The net effect of the electric field is that in addition to the random motion of the charged particles within a conductor, there is also a very small net motion or *drift* of the moving charged particles as a group in the direction of the electric force.

This motion is described in terms of the *drift* velocity  $\bar{v}_d$  of the particles.

Direct Current Circuits

#### Drift Velocity



 $\Delta Q = Nev_d A \Delta t \quad N = \text{ concentration of charges } (m^{-3})$ 

$$I = \frac{\Delta Q}{\Delta t} = Nev_d A$$

Direct Current Circuits

#### **Current Density**

The current *per unit cross-section area* is called the current density *J*.

$$J = \frac{I}{A} = \frac{Nev_d A}{A}$$

$$J = Nev_{d}$$

The electric field E in terms of current density J is:

$$E = \rho J$$

The constant  $\rho$  is called the *resistivity* of the material.

Direct Current Circuits

#### Batteries (emf)

In order to produce an electric current in a circuit, a potential difference is needed. Batteries are one way of providing a difference in potential (called *electromotive force* or *emf*).

**€** \_⊣⊢\_\_

Direct Current Circuits

7

9

#### Ohm's Law

Georg Ohm (1787-1854)

- Current depends upon the conductivity of the material.
- It is more common to talk about *resistance R* (inverse of conductivity) and express this relationship as:

$$I = \frac{\Delta V}{R} \text{ or } \Delta V = I \cdot R$$

• The unit for resistance is called the *ohm* and is abbreviated  $\Omega$  (omega)

Direct Current Circuits

**Schematic Diagrams** 



The *direction of current* is by convention the *direction a positive charge moves* through the circuit, which is towards the negative terminal of the battery.

Direct Current Circuits	
-------------------------	--

#### Voltage



Direct Current Circuits

10

8

#### **Terminal Voltage**

The potential difference in a real battery is not equal to the emf due to *internal resistance* within the battery. This lowers the voltage available to the circuit.





Direct Current Circuits

11

# Resistance (R) and Resistivity ( $\rho$ )

It can be experimentally determined that the resistance of a wire is directly proportional to its length l and inversely proportional to its cross-sectional area A.



The proportionality constant  $\rho$  is called the *resistivity* and depends upon the material used for the wire.

#### $\rho$ [=] $\Omega \cdot m$

Direct Current Circuits

#### **Electric Power**

To find the power transformed by an electric device recall that energy is  $Q\Delta V$ . Power is the rate energy is transformed in the device or:

$$P = \frac{Q\Delta V}{t} = I\Delta V \qquad P = I\Delta V$$

13

The SI unit for power is a J/s or watt (1 W = 1 J/s). For resistors, combining the above with Ohm's Law results in:



Direct Current Circuits

## **Measuring Voltage**

• Voltmeters placed in series will block the current and create an open circuit.



**Measuring Voltage** 

- Voltmeters are placed in parallel with the points between which the voltage measurement is made
- Voltmeters have a very high resistance and do not affect the circuit (they draw a very small current)



Direct Current Circuits

14

## **Measuring Current**

- Ammeters are placed in series with the device ٠ through which the current measurement is made
- Ammeters have a very low resistance and do not affect the circuit (the voltage drop is very low)



## **Resistors in Series**



$$V_{ab} = \Delta V_1 + \Delta V_2 + \Delta V_3 = IR_1 + IR_2 + IR_3$$
$$V_{ab} = I(R_1 + R_2 + R_3)$$
$$I = \frac{V_{ab}}{R_1 + R_2 + R_3} = \frac{V_{ab}}{R_s}$$

**Measuring Current** 

• Ammeters placed in parallel will create a short circuit. Anything parallel to the meter will have no voltage across them and therefore no current



17

Direct Current Circuits

**Resistors in Series** 

$$\xrightarrow{I}$$

$$R_1 R_2 R_3$$

- *Current is the same* through each resistor and is the same as the current in the equivalent resistance
- Voltage drop across each resistor is different unless the resistance is the same:

$$R_s = \sum_i R_i$$
  
Direct Current Circuits

19

21

23

**Resistors in Series (Voltage Divider)** 



$$\Delta V_1 = IR_1 = \frac{V_{ab}R_1}{R_1 + R_2} \qquad \Delta V_2 = IR_2 = \frac{V_{ab}R_2}{R_1 + R_2}$$

Direct Current Circuits

20

#### **Resistors in Parallel**







- *Voltage drop is the same* across each resistor and the same as the voltage drop across the equivalent resistance
- Current is different through each resistor, the higher the resistance the lower the current



22

## **Resistors in Parallel (Current Divider)**

$$\frac{I}{b} \xrightarrow{I_1} R_1$$

$$\frac{I}{R_1} \xrightarrow{I_2} R_1$$

$$\frac{I}{R_2} \xrightarrow{I_1} R_2$$

$$\frac{I}{R_2} = \frac{I}{R_1} + \frac{I}{R_2} = \frac{R_2 + R_1}{R_1 R_2} \quad \text{so} \quad R = \frac{R_1 R_2}{R_1 + R_2}$$

$$\text{and} \quad V_{ab} = I \cdot \left(\frac{R_1 R_2}{R_1 + R_2}\right)$$

$$I_1 = \frac{V_{ab}}{R_1} = I \cdot \left(\frac{R_2}{R_1 + R_2}\right) \quad \text{and} \quad I_2 = \frac{V_{ab}}{R_2} = I \cdot \left(\frac{R_1}{R_1 + R_2}\right)$$

Direct Current Circuits

# Kirchhoff's Rules

1.) Junction Rule (Conservation of charge)

At any junction point, the sum of all currents entering the junction must equal the sum of all currents leaving the junction.



Direct Current Circuits

## **Kirchhoff's Rules**

2.) *Loop Rule* (Conservation of energy) The sum of the changes in potential around any closed path of a circuit is zero.



Direct Current Circuits

#### Galvanometers

- A *galvanometer* is simply a meter that deflects in proportion to the current running through it.
- The maximum deflection is called the full-scale deflection.
- · The key characteristics of a galvanometer are
  - The current  $I_{fs}$  required for full-scale deflection.
  - The resistance  $R_c$  of the coil of wire in the meter.

$$\overrightarrow{\Delta V = IR_c \ G} R_c$$



26

#### Voltmeters

A *voltmeter* consists of a resistor put in series with a galvanometer. The value of this resistance  $R_s$  determines the full-scale reading of the meter  $\Delta V_v$ .



27

25

#### Some Tips

- 1.) The decrease in voltage between the two ends of a resistor is called a *voltage drop*  $(V_R < 0)$ .
- 2.) Batteries provide an increase in potential difference.
- 3.) Label currents in each branch or loop with a symbol and arrow indicating the direction of the current. Let the algebra take care of the sign of the current. If you get a negative current it simply means it is in the opposite direction of what you assumed.

Direct Current Circuits

## Ammeters

An *ammeter* consists of a resistor put in parallel (called a *shunt resistor* or *shunt*) with a galvanometer. The value of this resistance  $R_{sh}$  determines the fullscale reading of the meter  $I_a$ .



Direct Current Circuits





**RC** Circuits

Direct Current Circuits

31

## **RC** Circuits (Charging)

The charge on the capacitor varies according to:

$$q(t) = Q_f \left( 1 - \mathrm{e}^{-t/\mathrm{R}c} \right) = C \mathcal{E} \left( 1 - \mathrm{e}^{-t/\mathrm{R}c} \right)$$

The current at any time is given by:

$$i = \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}$$
$$\begin{bmatrix} i = I_0 e^{-t/RC} \end{bmatrix}$$

*RC* is called the *time constant* ( $\tau$ ) and is the time it takes the capacitor to become 63.2% charged.

Direct Current Circuits 34



## **RC** Circuits (Charging)







RC Circuits (Discharging)



## **RC** Circuits (Discharging)

The charge on the capacitor varies according to:

$$q = Q_0 e^{-t/RC}$$

The current at any time is given by:

$$i = -\frac{dq}{dt} = \frac{Q_o}{RC} e^{-t/RC}$$
$$\begin{bmatrix} i = I_o e^{-t/RC} \end{bmatrix}$$
Direct Current Circuits





## **RC** Circuits (Discharging)



Direct Current Circuits

41

39

## **RC** Circuits

## **Uncharged**

Charged capacitor has same voltage as the device that is electrically parallel to it.

Direct Current Circuits