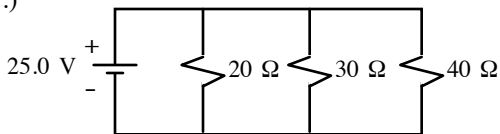


**AP Physics 1
Circuit Practice Problems**

- 1.) What voltage is applied to a $4.0\ \Omega$ resistor if the current is $1.5\ \text{A}$?
- 2.) A voltage of $75\ \text{V}$ is placed across a $15\ \Omega$ resistor. What is the current through the resistor?
- 3.) A resistor carries a current of $2.5\ \text{A}$ when connected to a $50\ \text{V}$ battery. What is the resistance of the resistor?
- 4.) Find the resistance of a $35.0\ \text{m}$ length of copper wire that is $2.00\ \text{mm}$ in diameter. Copper has a resistivity of $1.72 \times 10^{-8}\ \Omega \cdot \text{m}$.
- 5.) A lamp draws $0.50\ \text{A}$ from a $120\ \text{V}$ generator.
 - a.) How much power does the generator deliver?
 - b.) How much energy does the lamp convert to heat in 5.0 minutes?
- 6.) What is the maximum current that should be allowed in a $5.0\ \text{W}$, $220\ \Omega$ resistor?
- 7.) A heating coil has a resistance of $4.0\ \Omega$ and operates on $120\ \text{V}$.
 - a.) What is the current in the coil while it is operating?
 - b.) What energy is supplied to the coil in 5.0 minutes?
- 8.) A current of $1.2\ \text{A}$ flows through a $50\ \Omega$ resistor for 5.0 minutes. How much heat is generated by the resistor?
- 9.) Four $15\ \Omega$ resistors are connected in series with a $45\ \text{V}$ battery. What is the current in the circuit?
- 10.) Three resistors of $60.0\ \Omega$, $30.0\ \Omega$, and $20.0\ \Omega$ are connected in parallel across a $90.0\ \text{V}$ source. Find the current that is drawn from the source.


11.)



Consider the circuit to the left.

- a.) Find the equivalent resistance of the circuit
- b.) Find the power dissipated in the circuit.
- c.) Find the voltage across and current through each resistor.


12.)

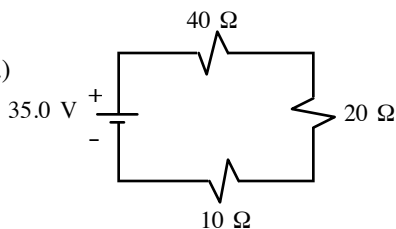

Consider the circuit to the left.

- a.) Find the equivalent resistance of the circuit
- b.) Find the power dissipated in the circuit.
- c.) Find the voltage across and current through each resistor.


13.)

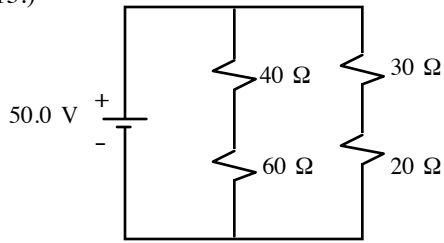

Consider the circuit to the left.

- Find the equivalent resistance of the circuit
- Find the voltage across and current through each resistor.


14.)

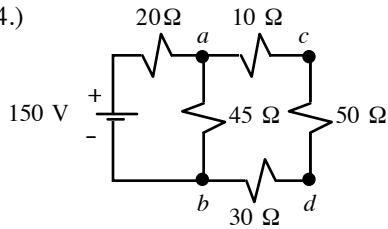

Consider the circuit to the left.

- Find the equivalent resistance of the circuit.
- Find the voltage across and current through each resistor.
- Find the potential differences V_{ad} , and V_{bc} .


15.)

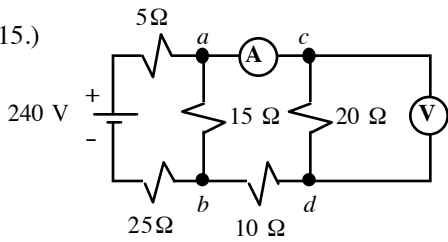

Consider the circuit to the left.

- Find the equivalent resistance of the circuit.
- What are the readings on the ammeter and voltmeter?

16.)

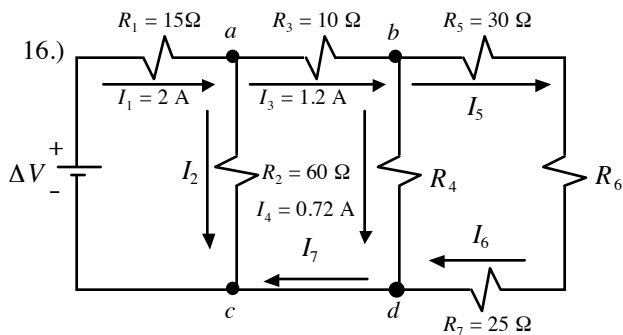

Consider the circuit to the left.

- Find the currents I_2 , I_5 , I_6 , and I_7 .
- Find the voltage ΔV and the resistances R_4 and R_6 .