

$$1.) \quad C = 500 \text{ pF}$$

$$Q = 0.326 \text{ } \mu\text{C}$$

$$d = 0.453 \text{ mm}$$

$$a.) \quad C = \frac{Q}{\Delta V} \text{ so } \Delta V = \frac{Q}{C} = \frac{0.326 \times 10^{-6} \text{ C}}{500 \times 10^{-12} \text{ F}} = \boxed{692 \text{ V}}$$

$$b.) \quad C = \frac{\epsilon_0 A}{d} \text{ so } A = \frac{Cd}{\epsilon_0} = \frac{(500 \times 10^{-12} \text{ F})(0.453 \times 10^{-3} \text{ m})}{\left(8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2}\right)}$$

$$A = \boxed{0.026 \text{ m}^2}$$


Check units:

$$A \text{ [=} \frac{(\text{F})(\text{m})}{\left(\frac{\text{C}^2}{\text{N} \cdot \text{m}^2}\right)} = \text{[=} \frac{\left(\frac{\text{C}}{\text{V}}\right)(\text{m})}{\left(\frac{\text{C}^2}{\text{J} \cdot \text{m}}\right)} \text{[=} \frac{\left(\frac{\text{C}}{\text{V}}\right)(\text{m})}{\left(\frac{\text{C}}{\text{V} \cdot \text{m}}\right)} \text{[=} \text{m}^2$$

$$c.) \quad E = \frac{\Delta V}{d} = \frac{692 \text{ V}}{0.453 \times 10^{-3} \text{ m}} = \boxed{1.53 \times 10^6 \frac{\text{V}}{\text{m}}}$$

$$d.) \quad \sigma = \frac{Q}{A} = \frac{0.326 \times 10^{-6} \text{ C}}{0.026 \text{ m}^2} = \boxed{13.3 \times 10^{-6} \frac{\text{C}}{\text{m}^2}}$$

2.) a.)

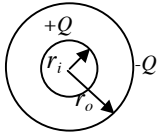

$$C = 150 \text{ pF}$$

$$r_i = 0.20 \text{ m}$$

Between the spheres: $E = \frac{Q}{4\pi\epsilon_0 r^2}$ (using Gauss's Law)

$$V_o - V_i = -\int_{r_i}^{r_o} \vec{E} \cdot d\vec{\ell} = -\int_{r_i}^{r_o} \frac{Q}{4\pi\epsilon_0 r^2} dr = \frac{Q}{4\pi\epsilon_0 r} \Bigg|_{r_i}^{r_o}$$

$$V_o - V_i = \frac{Q}{4\pi\epsilon_0} \left(\frac{1}{r_o} - \frac{1}{r_i} \right)$$

$$\frac{1}{C} = \frac{V_i - V_o}{Q} = \frac{1}{4\pi\epsilon_0} \left(\frac{1}{r_i} - \frac{1}{r_o} \right)$$

$$\frac{1}{r_o} = \frac{1}{r_i} - \frac{4\pi\epsilon_0}{C} \text{ so } \frac{1}{r_o} = \frac{C - 4\pi\epsilon_0 r_i}{Cr_i}$$

$$r_o = \frac{Cr_i}{C - 4\pi\epsilon_0 r_i} = \frac{(150 \times 10^{-12} \text{ F})(0.20 \text{ m})}{(150 \times 10^{-12} \text{ F}) - 4\pi \left(8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2}\right)(0.20 \text{ m})} = 0.235 \text{ m}$$

$$r_o - r_i = 0.235 \text{ m} - 0.20 \text{ m} = \boxed{0.035 \text{ m}}$$

2.)

b.)

$$Q = C\Delta V = (150 \times 10^{-12} \text{ F})(220 \text{ V}) = \boxed{3.3 \times 10^{-8} \text{ C}}$$

c.)

$$\text{inside: } A_i = 4\pi r_i^2 \quad \text{and} \quad \sigma_i = \frac{Q}{A_i} = \frac{(3.3 \times 10^{-8} \text{ C})}{4\pi(0.20 \text{ m})^2} = \boxed{6.57 \times 10^{-8} \frac{\text{C}}{\text{m}^2}}$$

$$\text{outside: } A_o = 4\pi r_o^2 \quad \text{and} \quad \sigma_o = \frac{Q}{A_o} = \frac{(-3.3 \times 10^{-8} \text{ C})}{4\pi(0.235 \text{ m})^2} = \boxed{-4.76 \times 10^{-8} \frac{\text{C}}{\text{m}^2}}$$

3.)

$$\Delta V = 140 \text{ V}, r_i = 12 \text{ cm}, r_o = 15 \text{ cm}$$

a.)

$$\text{From problem 2: } \frac{1}{C} = \frac{V_i - V_o}{Q} = \frac{1}{4\pi\epsilon_o} \left(\frac{1}{r_i} - \frac{1}{r_o} \right) \quad \text{so} \quad \frac{1}{C} = \frac{1}{4\pi\epsilon_o} \left(\frac{r_o - r_i}{r_i r_o} \right)$$

$$C = 4\pi\epsilon_o \left(\frac{r_i r_o}{r_o - r_i} \right) = 4\pi \left(8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2} \right) \frac{(0.15 \text{ m})(0.12 \text{ m})}{(0.15 \text{ m}) - (0.12 \text{ m})} = \boxed{66.7 \text{ pF}}$$

b.)


$$Q = C\Delta V = (66.7 \times 10^{-12} \text{ F})(140 \text{ V}) = 9.34 \times 10^{-9} \text{ C} \quad \text{and} \quad E = \frac{Q}{4\pi\epsilon_o r^2} \quad (\text{from Gauss's Law})$$

$$E = \frac{(9.34 \times 10^{-9} \text{ C})}{4\pi \left(8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2} \right) (0.121 \text{ m})^2} = \boxed{5734 \frac{\text{N}}{\text{C}}}$$

c.)

$$E = \frac{(9.34 \times 10^{-9} \text{ C})}{4\pi \left(8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2} \right) (0.149 \text{ m})^2} = \boxed{3781 \frac{\text{N}}{\text{C}}}$$

4.)

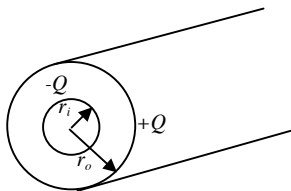

$$\begin{aligned} r_i &= 2.5 \text{ mm} \\ r_o &= 4.0 \text{ mm} \\ L &= 3.5 \text{ m} \\ V_{oi} &= 0.350 \text{ V} \end{aligned}$$

$$\text{a.) } E = \frac{\lambda}{2\pi\epsilon_o r} \quad (\text{using Gauss's Law})$$

$$V_o - V_i = -\int_{r_i}^{r_o} \vec{E} \cdot d\vec{\ell} = -\int_{r_i}^{r_o} \frac{\lambda}{2\pi\epsilon_o r} dr = -\left. \frac{\lambda}{2\pi\epsilon_o} \ln(r) \right|_{r_i}^{r_o}$$

$$V_o - V_i = \frac{\lambda_i}{2\pi\epsilon_o} (\ln(r_i) - \ln(r_o)) = \frac{\lambda_i}{2\pi\epsilon_o} \ln\left(\frac{r_i}{r_o}\right)$$

$$\lambda_i = \frac{2\pi\epsilon_o(V_o - V_i)}{\ln\left(\frac{r_i}{r_o}\right)} = \frac{2\pi \left(8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2} \right) (0.35 \text{ V} - 0)}{\ln\left(\frac{2.5 \text{ mm}}{4.0 \text{ mm}}\right)} = -4.14 \times 10^{-11} \frac{\text{C}}{\text{m}}$$

$$Q_i = \lambda_i L = \left(-4.14 \times 10^{-11} \frac{\text{C}}{\text{m}} \right) (3.5 \text{ m}) = \boxed{-1.45 \times 10^{-10} \text{ C}}$$


$$\begin{aligned} Q_i &= -1.45 \times 10^{-10} \text{ C} \\ Q_o &= 1.45 \times 10^{-10} \text{ C} \end{aligned}$$

$$b.) \quad V_o - V_i = \frac{\lambda}{2\pi\epsilon_o} (\ln(r_o) - \ln(r_i)) = \frac{\lambda}{2\pi\epsilon_o} \ln\left(\frac{r_o}{r_i}\right)$$

$$V_o - V_i = \frac{Q_i}{2\pi\epsilon_o L} \ln\left(\frac{r_o}{r_i}\right) \quad \text{so} \quad \frac{C}{L} = \frac{Q_i}{(V_o - V_i)L} = \frac{2\pi\epsilon_o}{\ln\left(\frac{r_o}{r_i}\right)}$$

$$\frac{C}{L} = \frac{2\pi \left(8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2}\right)}{\ln\left(\frac{4.0 \text{ mm}}{2.5 \text{ mm}}\right)} = \boxed{1.18 \times 10^{-10} \frac{\text{F}}{\text{m}}}$$

5.)

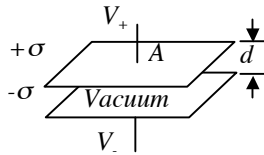

$$\begin{aligned} d &= 0.58 \text{ cm} \\ A &= (0.18 \text{ m})^2 = 0.0324 \text{ m}^2 \\ V_+ - V_- &= 50 \text{ V} \end{aligned}$$

a.)

$$C = \frac{\epsilon_o A}{d} = \frac{\left(8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2}\right) (0.0324 \text{ m}^2)}{(0.58 \times 10^{-2} \text{ m})} = \boxed{49.4 \text{ pF}}$$

Check units:

$$C [=] \frac{\left(\frac{\text{C}^2}{\text{N} \cdot \text{m}^2}\right) (0.0324 \text{ m}^2)}{(0.58 \times 10^{-2} \text{ m})} [=] \frac{\left(\frac{\text{C}^2}{\text{N}}\right)}{(\text{m})} [=] \frac{\left(\frac{\text{m} \cdot \text{C}}{\text{V}}\right)}{(\text{m})} [=] \frac{\text{C}}{\text{V}} [=] \text{ F}$$

b.)

$$C = \frac{Q}{\Delta V} \quad \text{so} \quad Q = C\Delta V = (49.4 \times 10^{-12} \text{ F})(50 \text{ V}) = \boxed{2.47 \times 10^{-9} \text{ C}}$$

c.)

$$\text{for uniform } E\text{-fields} \quad V_{+-} = E \cdot d \quad \text{so} \quad E = \frac{\Delta V}{d} = \frac{(50 \text{ V})}{(0.58 \times 10^{-2} \text{ m})} = \boxed{8.62 \times 10^3 \frac{\text{V}}{\text{m}}}$$

d.)

$$U_C = \frac{1}{2} Q\Delta V = \frac{1}{2} (2.47 \times 10^{-9} \text{ C})(50 \text{ V}) = \boxed{6.18 \times 10^{-8} \text{ J}}$$

Check units:

$$U_C [=] \text{ C} \cdot \Delta V [=] \text{ C} \cdot \frac{\text{J}}{\text{C}} [=] \text{ J}$$

5.)

e.) When battery is disconnected the charge cannot change so when $d = 1.16$ cm:

$$Q = 2.47 \times 10^{-9} \text{ C}$$

$$C = \frac{\epsilon_0 A}{d} = \frac{\left(8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2}\right) (0.0324 \text{ m}^2)}{(1.16 \times 10^{-2} \text{ m})} = 24.7 \text{ pF}$$

$$C = \frac{Q}{\Delta V} \quad \text{so} \quad \Delta V = \frac{Q}{C} = \frac{(2.47 \times 10^{-9} \text{ C})}{(24.7 \times 10^{-12} \text{ F})} = 100 \text{ V}$$

$$E = \frac{\Delta V}{d} = \frac{(100 \text{ V})}{(1.16 \times 10^{-2} \text{ m})} = 8.62 \times 10^3 \frac{\text{V}}{\text{m}}$$

$$U_C = \frac{1}{2} Q \Delta V = \frac{1}{2} (2.47 \times 10^{-9} \text{ C})(100 \text{ V}) = 1.24 \times 10^{-7} \text{ J}$$

6.) When battery remains connected voltage is fixed and the charge can change so when $d = 1.16$ cm:

a.) as in (5e):

$$C = 24.7 \text{ pF}$$

b.)

$$Q = C \Delta V = (24.7 \times 10^{-12} \text{ F})(50 \text{ V}) = 1.235 \times 10^{-9} \text{ C}$$

c.)


$$E = \frac{\Delta V}{d} = \frac{(50 \text{ V})}{(1.16 \times 10^{-2} \text{ m})} = 4.31 \times 10^3 \frac{\text{V}}{\text{m}}$$

d.)

$$U_C = \frac{1}{2} Q \Delta V = \frac{1}{2} (1.235 \times 10^{-9} \text{ C})(50 \text{ V}) = 3.09 \times 10^{-8} \text{ J}$$


7.)

a.)

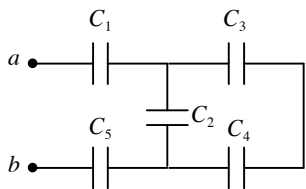


C_3 is in series with C_4 so they can be replaced by their equivalent.
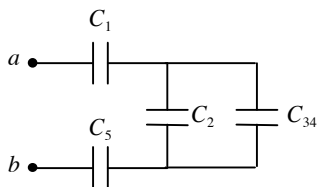
$$\frac{1}{C_{34}} = \frac{1}{C_3} + \frac{1}{C_4} = \frac{1}{2.3 \mu\text{F}} + \frac{1}{2.3 \mu\text{F}} \quad \text{and} \quad C_{34} = 1.15 \mu\text{F}$$




C_{34} is in parallel with C_2 so they can be replaced by their equivalent.
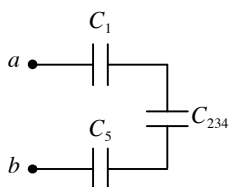
$$C_{234} = C_2 + C_{34} = 2.3 \mu\text{F} + 1.15 \mu\text{F} \quad \text{and} \quad C_{234} = 3.45 \mu\text{F}$$



C_1 , C_{234} , and C_5 are all in series so they can be replaced by their equivalent.

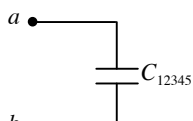
$$\frac{1}{C_{12345}} = \frac{1}{C_1} + \frac{1}{C_{234}} + \frac{1}{C_5} = \frac{1}{4.6 \mu\text{F}} + \frac{1}{3.45 \mu\text{F}} + \frac{1}{4.6 \mu\text{F}} \quad \text{and} \quad C_{12345} = 1.38 \mu\text{F}$$



So the equivalent capacitance is $C_{eq} = 1.38 \mu\text{F}$

7.)

b.)

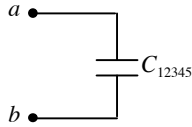


The charge on the equivalent capacitance is the charge on C_1 , C_5 , and C_{234} since capacitors in series have the same charge and the same charge as their equivalent.

$$Q_{12345} = C_{12345} \Delta V_{ab} = (1.38 \times 10^{-6} \text{ F})(540 \text{ V}) = 7.452 \times 10^{-4} \text{ C}$$

so $Q_1 = Q_5 = Q_{234} = 7.452 \times 10^{-4} \text{ C}$

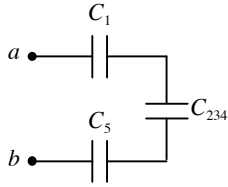
and $\Delta V_1 = \frac{Q_1}{C_1} = \frac{(7.452 \times 10^{-4} \text{ C})}{(4.6 \times 10^{-6} \text{ F})} = 162 \text{ V}$ and $\Delta V_5 = \frac{Q_5}{C_5} = \frac{(7.452 \times 10^{-4} \text{ C})}{(4.6 \times 10^{-6} \text{ F})} = 162 \text{ V}$



The voltage on the equivalent C_{234} is the same as the voltage on C_2 and the equivalent C_{34} since capacitors in parallel have the same voltage and the same voltage as their equivalent.

so $\Delta V_2 = \Delta V_{34} = \Delta V_{234} = \frac{Q_{234}}{C_{234}} = \frac{(7.452 \times 10^{-4} \text{ C})}{(3.45 \times 10^{-6} \text{ F})} = 216 \text{ V}$

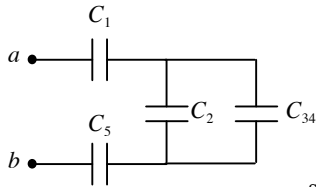and $Q_2 = C_2 \Delta V_2 = (2.3 \times 10^{-6} \text{ F})(216 \text{ V}) = 4.968 \times 10^{-4} \text{ C}$



The charge on the equivalent C_{34} is the same as the charge on C_3 and C_4 since capacitors in series have the same charge and the same charge as their equivalent.


so $Q_3 = Q_4 = Q_{34} = C_{34} \Delta V_{34} = (1.15 \times 10^{-6} \text{ F})(216 \text{ V}) = 2.484 \times 10^{-4} \text{ C}$

and $\Delta V_3 = \frac{Q_3}{C_3} = \frac{(2.484 \times 10^{-4} \text{ C})}{(2.3 \times 10^{-6} \text{ F})} = 108 \text{ V}$ and $\Delta V_4 = \frac{Q_4}{C_4} = \frac{(2.484 \times 10^{-4} \text{ C})}{(2.3 \times 10^{-6} \text{ F})} = 108 \text{ V}$

To summarize:


Capacitor	Capacitance	Charge	Voltage
C_1	$4.6 \times 10^{-6} \text{ F}$	$7.452 \times 10^{-4} \text{ C}$	162 V
C_2	$2.3 \times 10^{-6} \text{ F}$	$4.968 \times 10^{-4} \text{ C}$	216 V
C_3	$2.3 \times 10^{-6} \text{ F}$	$2.484 \times 10^{-4} \text{ C}$	108 V
C_4	$2.3 \times 10^{-6} \text{ F}$	$2.484 \times 10^{-4} \text{ C}$	108 V
C_5	$4.6 \times 10^{-6} \text{ F}$	$7.452 \times 10^{-4} \text{ C}$	162 V

1.)

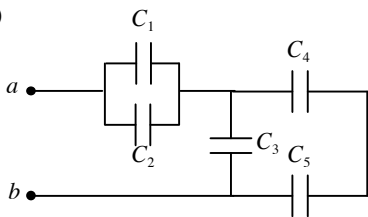


$$C_1 = C_2 = 5.0 \mu\text{F} \text{ and } C_3 = C_4 = C_5 = 10.0 \mu\text{F}, V_{ab} = 120 \text{ V}$$

a.)

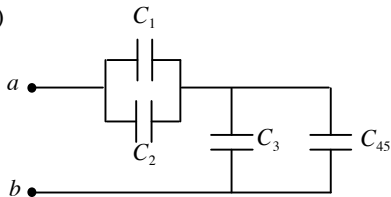


C_4 and C_5 are in series so they can be replaced by their equivalent.
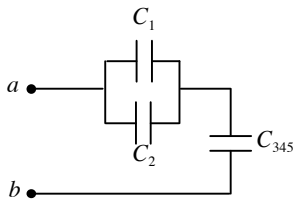
$$\frac{1}{C_{45}} = \frac{1}{C_4} + \frac{1}{C_5} = \frac{1}{10 \mu\text{F}} + \frac{1}{10 \mu\text{F}} \quad \text{and} \quad C_{45} = 5 \mu\text{F}$$




C_{45} and C_3 are in parallel so they can be replaced by their equivalent.
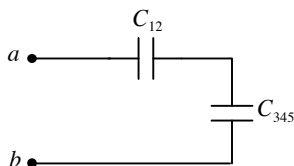
$$C_{345} = C_3 + C_{45} = 10 \mu\text{F} + 5 \mu\text{F} = 15 \mu\text{F}$$



C_1 and C_2 are in parallel so they can be replaced by their equivalent.

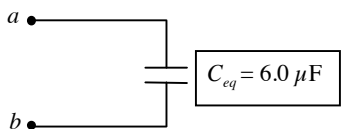
$$C_{12} = C_1 + C_2 = 5 \mu\text{F} + 5 \mu\text{F} = 10 \mu\text{F}$$



C_{12} and C_{345} are in series so they can be replaced by their equivalent.

$$\frac{1}{C_{12345}} = \frac{1}{C_{12}} + \frac{1}{C_{345}} = \frac{1}{10 \mu\text{F}} + \frac{1}{15 \mu\text{F}} \quad \text{and} \quad C_{12345} = 6 \mu\text{F}$$


b.)

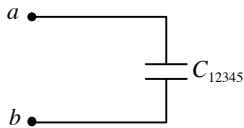

The charge on the equivalent capacitance is the charge on C_1 , C_5 , and C_{234} since capacitors in series have the same charge and the same charge as their equivalent.

$$Q_{12345} = C_{12345} \Delta V_{ab} = (6.0 \times 10^{-6} \text{ F})(120 \text{ V}) = 7.20 \times 10^{-4} \text{ C}$$

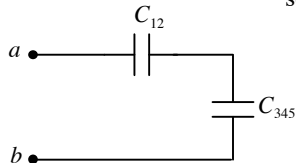so $Q_{12} = Q_{345} = 7.20 \times 10^{-4} \text{ C}$




The voltage on the equivalent C_1 is the same as the voltage on C_2 and the equivalent C_{12} since capacitors in parallel have the same voltage and the same voltage as their equivalent.

$$\Delta V_1 = \Delta V_2 = \Delta V_{12} = \frac{Q_{12}}{C_{12}} = \frac{7.20 \times 10^{-4} \text{ C}}{10 \times 10^{-6} \text{ F}} = 72 \text{ V}$$

It follows that:

$$Q_1 = C_1 \Delta V_1 = (5.0 \times 10^{-6} \text{ F})(72 \text{ V}) = 3.60 \times 10^{-4} \text{ C}$$

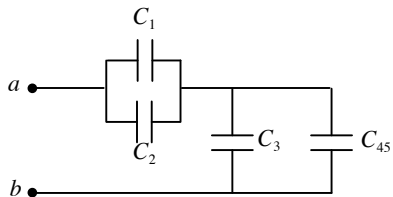and $Q_2 = C_2 \Delta V_2 = (5.0 \times 10^{-6} \text{ F})(72 \text{ V}) = 3.60 \times 10^{-4} \text{ C}$




HO 35 Solutions

Also: $\Delta V_{345} = \frac{Q_{345}}{C_{345}} = \frac{(7.2 \times 10^{-4} \text{ C})}{(15 \times 10^{-6} \text{ F})} = 48 \text{ V}$ which is the voltage on C_3 and C_45 since they are in parallel and

have the same voltage as their equivalent C_{345} . It follows that:
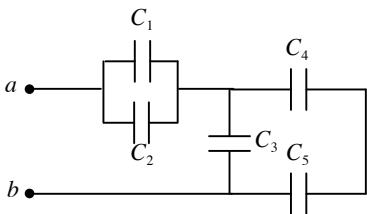
$$Q_3 = C_3 \Delta V_3 = (10.0 \times 10^{-6} \text{ F})(48 \text{ V}) = 4.80 \times 10^{-4} \text{ C} \quad \text{and} \quad Q_{45} = C_{45} \Delta V_{45} = (5.0 \times 10^{-6} \text{ F})(48 \text{ V}) = 2.40 \times 10^{-4} \text{ C}$$



Finally the charge on C_4 and C_5 are the same as their equivalent C_{45} since they are in series and have the same charge and the same charge as their equivalent. Therefore:

$$\Delta V_4 = \frac{Q_4}{C_4} = \frac{(2.40 \times 10^{-4} \text{ C})}{(10.0 \times 10^{-6} \text{ F})} = 24 \text{ V} \quad \text{and} \quad \Delta V_5 = \frac{Q_5}{C_5} = \frac{(2.40 \times 10^{-4} \text{ C})}{(10.0 \times 10^{-6} \text{ F})} = 24 \text{ V}$$


To summarize:

Capacitor	Capacitance	Charge	Voltage
C_1	$5.0 \times 10^{-6} \text{ F}$	$3.60 \times 10^{-4} \text{ C}$	72 V
C_2	$5.0 \times 10^{-6} \text{ F}$	$3.60 \times 10^{-4} \text{ C}$	72 V
C_3	$10 \times 10^{-6} \text{ F}$	$4.80 \times 10^{-4} \text{ C}$	48 V
C_4	$10 \times 10^{-6} \text{ F}$	$2.40 \times 10^{-4} \text{ C}$	24 V
C_5	$10 \times 10^{-6} \text{ F}$	$2.40 \times 10^{-4} \text{ C}$	24 V


$$\text{c.) } U_C = \frac{1}{2} Q_{eq} V_{ab} = \frac{1}{2} C_{eq} V_{ab}^2 = \frac{1}{2} (6.0 \times 10^{-6} \text{ C})(120 \text{ V})^2 = \boxed{4.32 \times 10^{-2} \text{ J}}$$

2.)

a.)

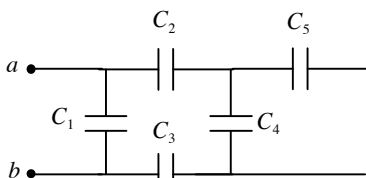


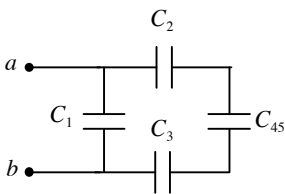$C_1 = C_2 = C_3 = C_4 = C_5 = 5.0 \mu\text{F}$. The potential difference between a and b is 100 V.




C_4 and C_5 are in parallel and can be replaced by their equivalent C_{45} .
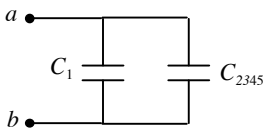
$$C_{45} = C_4 + C_5 = 5.0 \mu\text{F} + 5.0 \mu\text{F} = 10 \mu\text{F}$$



C_2 , C_3 , and C_{45} are in series and can be replaced by their equivalent C_{2345} .

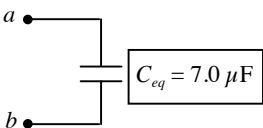
$$\frac{1}{C_{2345}} = \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_{45}} = \frac{1}{5.0 \mu\text{F}} + \frac{1}{5.0 \mu\text{F}} + \frac{1}{10 \mu\text{F}} \quad \text{and} \quad C_{2345} = 2.0 \mu\text{F}$$



C_1 and C_{2345} are in parallel and can be replaced by their equivalent C_{12345} .

$$C_{eq} = C_{12345} = C_1 + C_{2345} = 5.0 \mu\text{F} + 2.0 \mu\text{F} = 7.0 \mu\text{F}$$

2.)

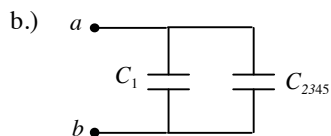


The voltage on the equivalent capacitance is the voltage on C_1 and C_{2345} since capacitors in parallel have the same voltage and the same voltage as their equivalent.

$$\Delta V_{12345} = \Delta V_1 = \Delta V_{2345} = V_{ab} = 100 \text{ V}$$

so $Q_1 = C_1 V_1 = (5.0 \times 10^{-6} \text{ F})(100 \text{ V}) = 5.00 \times 10^{-4} \text{ C}$

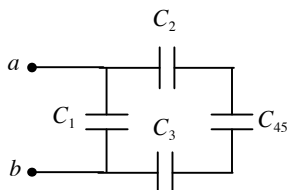and $Q_{2345} = C_{2345} V_{2345} = (2.0 \times 10^{-6} \text{ F})(100 \text{ V}) = 2.00 \times 10^{-4} \text{ C}$




The charge on C_2 , C_{45} , and C_3 is the same since they are in series and the same charge as their equivalent C_{2345} .

$$Q_2 = Q_{45} = Q_3 = Q_{2345} = 2.00 \times 10^{-4} \text{ C}$$

so $\Delta V_2 = \frac{Q_2}{C_2} = \frac{(2.00 \times 10^{-4} \text{ C})}{(5.0 \times 10^{-6} \text{ F})} = 40 \text{ V}$ and $\Delta V_3 = \frac{Q_3}{C_3} = \frac{(2.00 \times 10^{-4} \text{ C})}{(5.0 \times 10^{-6} \text{ F})} = 40 \text{ V}$

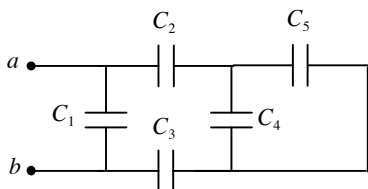also $\Delta V_{45} = \frac{Q_{45}}{C_{45}} = \frac{(2.00 \times 10^{-4} \text{ C})}{(10.0 \times 10^{-6} \text{ F})} = 20 \text{ V}$



The voltage on C_4 and C_5 are the same and equal to the voltage on their equivalent C_{45} because they are in parallel.

$$\Delta V_4 = \Delta V_5 = \Delta V_{45} = 20 \text{ V}$$

so $Q_4 = C_4 V_4 = (5.0 \times 10^{-6} \text{ F})(20 \text{ V}) = 1.00 \times 10^{-4} \text{ C}$

$$Q_5 = C_5 V_5 = (5.0 \times 10^{-6} \text{ F})(20 \text{ V}) = 1.00 \times 10^{-4} \text{ C}$$


To summarize:

Capacitor	Capacitance	Charge	Voltage
C_1	$5.0 \times 10^{-6} \text{ F}$	$5.0 \times 10^{-4} \text{ C}$	100 V
C_2	$5.0 \times 10^{-6} \text{ F}$	$2.0 \times 10^{-4} \text{ C}$	40 V
C_3	$5.0 \times 10^{-6} \text{ F}$	$2.0 \times 10^{-4} \text{ C}$	40 V
C_4	$5.0 \times 10^{-6} \text{ F}$	$1.0 \times 10^{-4} \text{ C}$	20 V
C_5	$5.0 \times 10^{-6} \text{ F}$	$1.0 \times 10^{-4} \text{ C}$	20 V

c.) $U_C = \frac{1}{2} Q_{eq} V_{ab} = \frac{1}{2} C_{eq} V_{ab}^2 = \frac{1}{2} (7.0 \times 10^{-6} \text{ C})(100 \text{ V})^2 = \boxed{3.50 \times 10^{-2} \text{ J}}$


HO 35 Solutions

3.)

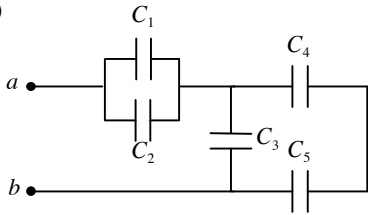


$$C_1 = C_5 = 6.0 \mu\text{F}, C_3 = 3.6 \mu\text{F} \text{ and } C_2 = C_4 = 4.0 \mu\text{F}, V_{ab} = 120 \text{ V}$$

a.)

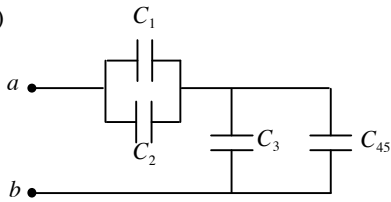


C_4 and C_5 are in series so they can be replaced by their equivalent.
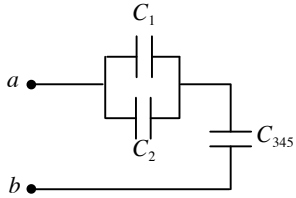
$$\frac{1}{C_{45}} = \frac{1}{C_4} + \frac{1}{C_5} = \frac{1}{4.0 \mu\text{F}} + \frac{1}{6.0 \mu\text{F}} \text{ and } C_{45} = 2.4 \mu\text{F}$$




C_{45} and C_3 are in parallel so they can be replaced by their equivalent.
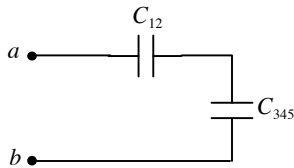
$$C_{345} = C_3 + C_{45} = 3.6 \mu\text{F} + 2.4 \mu\text{F} = 6.0 \mu\text{F}$$



C_1 and C_2 are in parallel so they can be replaced by their equivalent.

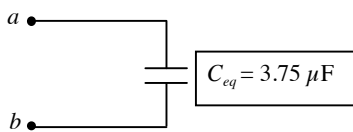
$$C_{12} = C_1 + C_2 = 6.0 \mu\text{F} + 4.0 \mu\text{F} = 10 \mu\text{F}$$



C_{12} and C_{345} are in series so they can be replaced by their equivalent.

$$\frac{1}{C_{12345}} = \frac{1}{C_{12}} + \frac{1}{C_{345}} = \frac{1}{10 \mu\text{F}} + \frac{1}{6.0 \mu\text{F}} \text{ and } C_{12345} = 3.75 \mu\text{F}$$


b.)

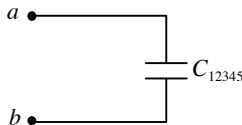

The charge on the equivalent capacitance is the charge on C_{12} , C_5 , and C_{234} since capacitors in series have the same charge and the same charge as their equivalent.

$$Q_{12345} = C_{12345} V_{ab} = (3.75 \times 10^{-6} \text{ F})(120 \text{ V}) = 4.5 \times 10^{-4} \text{ C}$$

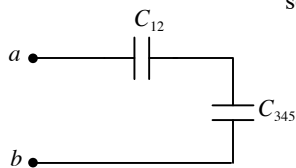
so $Q_{12} = Q_{345} = 4.5 \times 10^{-4} \text{ C}$



The voltage on the equivalent C_1 is the same as the voltage on C_2 and the equivalent C_{12} since capacitors in parallel have the same voltage and the same voltage as their equivalent.

$$\Delta V_1 = \Delta V_2 = \Delta V_{12} = \frac{Q_{12}}{C_{12}} = \frac{4.5 \times 10^{-4} \text{ C}}{10 \times 10^{-6} \text{ F}} = 45 \text{ V}$$

It follows that:

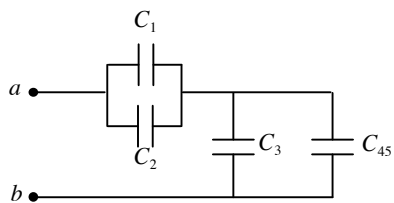

$$Q_1 = C_1 \Delta V_1 = (6.0 \times 10^{-6} \text{ F})(45 \text{ V}) = 2.70 \times 10^{-4} \text{ C}$$


and $Q_2 = C_2 \Delta V_2 = (4.0 \times 10^{-6} \text{ F})(45 \text{ V}) = 1.80 \times 10^{-4} \text{ C}$

HO 35 Solutions

Also: $\Delta V_{345} = \frac{Q_{345}}{C_{345}} = \frac{(4.5 \times 10^{-4} \text{ C})}{(6.0 \times 10^{-6} \text{ F})} = 75 \text{ V}$ which is the voltage on C_3 and C_{45} since they are in parallel and

have the same voltage as their equivalent C_{345} . It follows that:
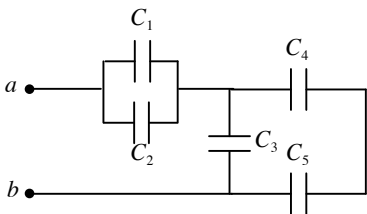
$$Q_3 = C_3 \Delta V_3 = (3.6 \times 10^{-6} \text{ F})(75 \text{ V}) = 2.70 \times 10^{-4} \text{ C} \quad \text{and} \quad Q_{45} = C_{45} \Delta V_{45} = (2.4 \times 10^{-6} \text{ F})(75 \text{ V}) = 1.80 \times 10^{-4} \text{ C}$$



Finally the charge on C_4 and C_5 are the same as their equivalent C_{45} since they are in series and have the same charge and the same charge as their equivalent. Therefore:


$$\Delta V_4 = \frac{Q_4}{C_4} = \frac{(1.80 \times 10^{-4} \text{ C})}{(4.0 \times 10^{-6} \text{ F})} = 45 \text{ V} \quad \text{and} \quad \Delta V_5 = \frac{Q_5}{C_5} = \frac{(1.80 \times 10^{-4} \text{ C})}{(6.0 \times 10^{-6} \text{ F})} = 30 \text{ V}$$

To summarize:

Capacitor	Capacitance	Charge	Voltage
C_1	$6.0 \times 10^{-6} \text{ F}$	$2.7 \times 10^{-4} \text{ C}$	45 V
C_2	$4.0 \times 10^{-6} \text{ F}$	$1.8 \times 10^{-4} \text{ C}$	45 V
C_3	$3.6 \times 10^{-6} \text{ F}$	$2.7 \times 10^{-4} \text{ C}$	75 V
C_4	$4.0 \times 10^{-6} \text{ F}$	$1.8 \times 10^{-4} \text{ C}$	45 V
C_5	$6.0 \times 10^{-6} \text{ F}$	$1.8 \times 10^{-4} \text{ C}$	30 V

$$c.) \quad U_C = \frac{1}{2} Q_{eq} V_{ab} = \frac{1}{2} C_{eq} V_{ab}^2 = \frac{1}{2} (3.75 \times 10^{-6} \text{ C})(120 \text{ V})^2 = \boxed{2.70 \times 10^{-2} \text{ J}}$$

4.)

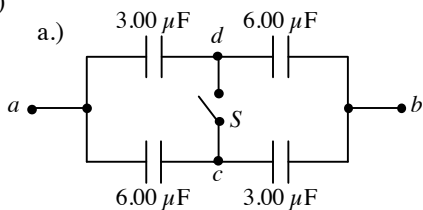



$$V_{ab} = 360 \text{ V}$$

With switch S open the two sets of $3.00 \mu\text{F}$ and $6.00 \mu\text{F}$ capacitors are in series and can be replaced by their equivalent.

$$\frac{1}{C_{36}} = \frac{1}{3.00 \mu\text{F}} + \frac{1}{6.00 \mu\text{F}} \quad \text{and} \quad C_{36} = 2.00 \mu\text{F}$$

These are in parallel and the equivalent capacitance is:
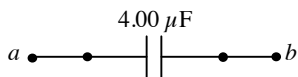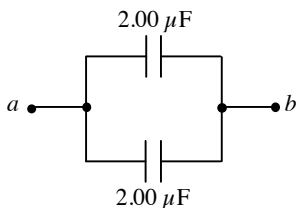
$$C_{eq} = 2.00 \mu\text{F} + 2.00 \mu\text{F} = 4.00 \mu\text{F}$$




The voltage on the $4.00 \mu\text{F}$ equivalent is the same as the voltage on the two $2.00 \mu\text{F}$ equivalents and is equal to $V_{ab} = 360 \text{ V}$. The charges are:

$$Q = C \Delta V = (2.00 \times 10^{-6} \text{ F})(360 \text{ V}) = 7.20 \times 10^{-4} \text{ C}$$

This is the charge on the $3.00 \mu\text{F}$ and $6.00 \mu\text{F}$ capacitors since they are in series. There voltages are:
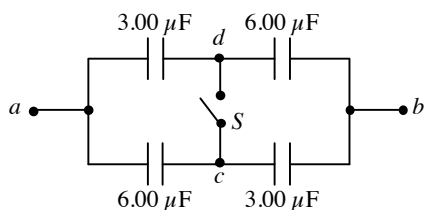
$$\Delta V_3 = \frac{Q_3}{C_3} = \frac{(7.20 \times 10^{-4} \text{ C})}{(3.00 \times 10^{-6} \text{ F})} = 240 \text{ V} \quad \text{and} \quad \Delta V_6 = \frac{Q_6}{C_6} = \frac{(7.20 \times 10^{-4} \text{ C})}{(6.00 \times 10^{-6} \text{ F})} = 120 \text{ V}$$




HO 35 Solutions

If $V_b = 0$ then $V_a = 360 \text{ V}$ and $V_d = V_a - V_3 = 360 \text{ V} - 240 \text{ V} = 120 \text{ V}$ and $V_c = V_a - V_6 = 360 \text{ V} - 240 \text{ V} = 120 \text{ V}$.


Therefore: $V_{cd} = V_c - V_d = 240 \text{ V} - 120 \text{ V} = 120 \text{ V}$

b.)

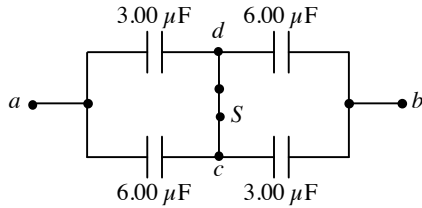


With switch S closed the two sets of $3.00 \mu\text{F}$ and $6.00 \mu\text{F}$ capacitors are in parallel and can be replaced by their equivalent.
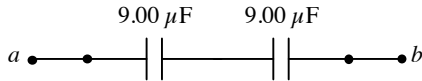
$$C_{36} = 3.00 \mu\text{F} + 6.00 \mu\text{F} = 9.00 \mu\text{F}$$



The two $9.00 \mu\text{F}$ equivalents are in series so the equivalent capacitance is:
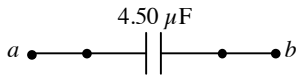
$$\frac{1}{C_{eq}} = \frac{1}{9.00 \mu\text{F}} + \frac{1}{9.00 \mu\text{F}} \quad \text{and} \quad C_{eq} = 4.50 \mu\text{F}$$



The charge on the two $9.00 \mu\text{F}$ equivalents is the same as the charge on the $4.50 \mu\text{F}$ equivalent capacitance.

$$Q = C\Delta V = (4.50 \times 10^{-6} \text{ F})(360 \text{ V}) = 1.62 \times 10^{-4} \text{ C}$$

The voltages on the $9.00 \mu\text{F}$ equivalents are the same: $\Delta V_9 = \frac{Q_9}{C_9} = \frac{(1.62 \times 10^{-4} \text{ C})}{(9.00 \times 10^{-6} \text{ F})} = 180 \text{ V}$

This is the voltage on the $3.00 \mu\text{F}$ and $6.00 \mu\text{F}$ capacitors because they are in parallel and all capacitors have voltages $\Delta V = 180 \text{ V}$.

c.) Based upon equivalent capacitances:

$$Q_a = C_{eq} V_{ab} = (4.00 \times 10^{-6} \text{ F})(360 \text{ V}) = 1.44 \times 10^{-3} \text{ C}$$

$$Q_b = C_{eq} V_{ab} = (4.50 \times 10^{-6} \text{ F})(360 \text{ V}) = 1.62 \times 10^{-3} \text{ C}$$

and the charge that flows through switch S is: $Q_b - Q_a = 1.62 \times 10^{-3} \text{ C} - 1.44 \times 10^{-3} \text{ C} = 1.80 \times 10^{-4} \text{ C}$

5.) Cylindrical air capacitor $L = 25.0 \text{ m}$ and $U_c = 5.40 \times 10^{-9} \text{ J}$ when $V = 3.00 \text{ V}$

a.) $U_c = \frac{1}{2} Q\Delta V$ so $Q = \frac{2U_c}{\Delta V} = \frac{2(5.40 \times 10^{-9} \text{ J})}{(3.00 \text{ V})} = 3.6 \times 10^{-9} \text{ C}$

b.) for cylindrical capacitors

$$\Delta V = \frac{Q}{2\pi\epsilon_0 L} \ln\left(\frac{r_o}{r_i}\right) \text{ so } \ln\left(\frac{r_o}{r_i}\right) = \frac{2\pi\epsilon_0 L\Delta V}{Q} \quad \text{and} \quad \frac{r_o}{r_i} = \exp\left(\frac{2\pi\epsilon_0 L\Delta V}{Q}\right)$$

$$\frac{r_o}{r_i} = \exp\left(\frac{2\pi\left(8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N}\cdot\text{m}^2}\right)(25 \text{ m})(3.00 \text{ V})}{(3.6 \times 10^{-9} \text{ C})}\right) = 3.19 \quad \text{and} \quad \frac{r_i}{r_o} = 0.314$$

6.)

parallel-plate capacitor with dielectric constant $\kappa = 3.40$ and dielectric strength $E = 2.00 \times 10^7$ V/mcapacitance $C = 1.37$ nF and voltage must be at least $\Delta V = 6000$ V.

$$\Delta V = E \cdot d \quad \text{so} \quad d = \frac{\Delta V}{E} = \frac{(6000 \text{ V})}{\left(2.00 \times 10^7 \frac{\text{V}}{\text{m}}\right)} = 3.00 \times 10^{-4} \text{ m}$$

$$C = \frac{\kappa \epsilon_0 A}{d} \quad \text{so} \quad A = \frac{Cd}{\kappa \epsilon_0} = \frac{(1.37 \times 10^{-9} \text{ F})(3.00 \times 10^{-4} \text{ m})}{3.4 \left(8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2}\right)} = \boxed{1.37 \times 10^{-2} \text{ m}^2}$$

7.) parallel-plate capacitor with $d = 1.60$ mm and dielectric constant $\kappa = 4.50$ and dielectric strength $E = 1.40 \times 10^6$ V/m

a.)

$$E = \frac{\sigma}{\kappa \epsilon_0} \quad \text{so} \quad \sigma = \kappa \epsilon_0 E = 4.50 \left(8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2}\right) \left(1.40 \times 10^6 \frac{\text{V}}{\text{m}}\right) = \boxed{5.58 \times 10^{-5} \frac{\text{C}}{\text{m}^2}}$$

b.)

$$\sigma_i = \sigma \left(1 - \frac{1}{\kappa}\right) = 5.58 \times 10^{-5} \frac{\text{C}}{\text{m}^2} \left(1 - \frac{1}{4.50}\right) = \boxed{4.34 \times 10^{-5} \frac{\text{C}}{\text{m}^2}}$$

8.) The two slabs are in series (they have the same charge density) with same area A and thickness $\frac{d}{2}$

$$C_1 = \frac{\kappa_1 \epsilon_0 A}{\frac{d}{2}} = \frac{2\kappa_1 \epsilon_0 A}{d} \quad \text{and} \quad C_2 = \frac{2\kappa_2 \epsilon_0 A}{d}$$

Since they are in series:

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{\frac{2\kappa_1 \epsilon_0 A}{d}} + \frac{1}{\frac{2\kappa_2 \epsilon_0 A}{d}} = \frac{d}{2\epsilon_0 A} \left(\frac{1}{\kappa_1} + \frac{1}{\kappa_2}\right) = \frac{d}{2\epsilon_0 A} \left(\frac{\kappa_2 + \kappa_1}{\kappa_1 \kappa_2}\right)$$

$$\boxed{C_{eq} = \frac{2\epsilon_0 A}{d} \left(\frac{\kappa_1 \kappa_2}{\kappa_2 + \kappa_1}\right)}$$