

HO 36 Solutions

- 1.)  $I = 4.8 \text{ A}$  for 2 hours

$$I = \frac{\Delta Q}{\Delta t} \quad \text{so} \quad \Delta Q = I \cdot \Delta t = (4.8 \text{ A})(7200 \text{ s}) = \left(4.8 \frac{\text{C}}{\text{s}}\right)(7200 \text{ s}) = \boxed{34,560 \text{ C}}$$

- 2.)  $\Delta Q = 72 \text{ C}$ ,  $\Delta t = 1 \text{ hr}$ ,  $n = 5.8 \times 10^{28} \text{ e}^-/\text{m}^3$ ,  $D = 1.3 \text{ mm}$

a.)  $I = \frac{\Delta Q}{\Delta t} = \frac{72 \text{ C}}{3600 \text{ s}} = \boxed{0.02 \text{ A}}$

b.)  $I = nqv_d A$  so  $v_d = \frac{I}{nqA} = \frac{(0.02 \text{ A})}{(5.8 \times 10^{28} \text{ m}^{-3})(1.6 \times 10^{-19} \text{ C})(\pi(0.65 \times 10^{-3} \text{ m})^2)} = \boxed{1.62 \times 10^{-6} \frac{\text{m}}{\text{s}}}$

- 3.)  $\ell = 35.0 \text{ m}$  and  $D = 2.06 \text{ mm}$

for copper  $\rho = 1.72 \times 10^{-8} \Omega \cdot \text{m}$   $R_{Cu} = \frac{\rho \ell}{A} = \frac{(1.72 \times 10^{-8} \Omega \cdot \text{m})(35 \text{ m})}{\pi(1.025 \times 10^{-3} \text{ m})^2} = \boxed{0.18 \Omega}$

for gold  $\rho = 2.44 \times 10^{-8} \Omega \cdot \text{m}$   $R_{Au} = \frac{\rho \ell}{A} = \frac{(2.44 \times 10^{-8} \Omega \cdot \text{m})(35 \text{ m})}{\pi(1.025 \times 10^{-3} \text{ m})^2} = \boxed{0.26 \Omega}$

for silver  $\rho = 1.47 \times 10^{-8} \Omega \cdot \text{m}$   $R_{Cu} = \frac{\rho \ell}{A} = \frac{(1.47 \times 10^{-8} \Omega \cdot \text{m})(35 \text{ m})}{\pi(1.025 \times 10^{-3} \text{ m})^2} = \boxed{0.16 \Omega}$

- 4.)  $D_{Cu} = 2.2 \text{ mm}$

$$\frac{R_{Cu}}{\ell} = \frac{\rho}{A} = \frac{(1.72 \times 10^{-8} \Omega \cdot \text{m})(35 \text{ m})}{\pi(1.1 \times 10^{-3} \text{ m})^2} = 4.52 \times 10^{-3} \frac{\Omega}{\text{m}}$$


$$\frac{R}{\ell} = \frac{\rho}{A} = \frac{\rho}{\pi \cdot r^2} \quad \text{so} \quad r = \sqrt{\frac{\rho \ell}{\pi \cdot R}} = \sqrt{\frac{(2.75 \times 10^{-8} \Omega \cdot \text{m})}{\pi(4.52 \times 10^{-3} \frac{\Omega}{\text{m}})}} = 1.39 \times 10^{-3} \text{ m}$$

$$D = 2r = 2(1.39 \times 10^{-3} \text{ m}) = \boxed{2.78 \times 10^{-3} \text{ m}}$$

- 5.)  $R = 1.00 \Omega$  for copper wire with diameter  $D = 0.750 \text{ mm}$  and length  $\ell$

$$R = \frac{\rho \ell}{A} \quad \text{so} \quad \ell = \frac{RA}{\rho} = \frac{(1.00 \Omega)\pi(0.375 \times 10^{-3} \text{ m})^2}{(1.72 \times 10^{-8} \Omega \cdot \text{m})} = \boxed{26 \text{ m}}$$

- 6.)

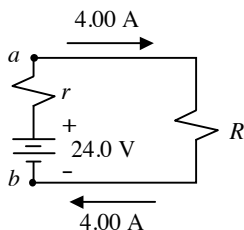


Terminal voltage is 20.2 V for the 24 V battery

a.)  $V_{ab} = \mathcal{E} - Ir$  so  $r = \frac{\mathcal{E} - V_{ab}}{I} = \frac{(24 \text{ V} - 20.2 \text{ V})}{4 \text{ A}} = \boxed{0.95 \Omega}$

b.)  $V_R = V_{ab} = 20.2 \text{ V}$  and  $V = IR$  or  $R = \frac{V}{I} = \frac{(20.2 \text{ V})}{(4 \text{ A})} = \boxed{5.05 \Omega}$

7.)

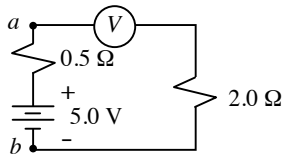


Ideal voltmeter has infinite resistance and there will be no current.

a.)  $I = 0$

b.)  $V_{ab} = \mathcal{E} - Ir = 5.0 \text{ V} - 0 = 5.0 \text{ V}$

c.) Voltmeter will read the terminal voltage of the battery  $V = V_{ab} = 5.0 \text{ V}$

8.)

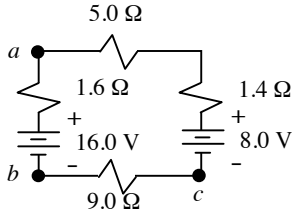

a.) Kirchoff's Loop rule:

 Going clockwise starting at  $b$ 

$$V_{16\text{V}} - V_{1.6\Omega} - V_{5.0\Omega} - V_{1.4\Omega} - V_{8\text{V}} - V_{9.0\Omega} = 0$$

$$16 \text{ V} - I(1.6 \Omega) - I(5.0 \Omega) - I(1.4 \Omega) - 8.0 \text{ V} - I(9.0 \Omega) = 0$$

$$8 \text{ V} - I(17 \Omega) = 0 \quad \text{and} \quad I = \frac{8 \text{ V}}{17 \Omega} = 0.471 \text{ A} \quad \text{and is clockwise}$$


b.)  $V_{ab} = \mathcal{E} - Ir = 16.0 \text{ V} - (0.471 \text{ A})(1.6 \Omega) = 15.25 \text{ V}$

 c.)  $V_{ac} = V_a - V_c$  making point  $c$  the reference point (i.e.  $V_c = 0$ ).

$$V_a = -I(9.0 \Omega) + 16 \text{ V} - I(1.6 \Omega) = 16 \text{ V} - (0.471 \text{ A})(10.6 \Omega) = 11.01 \text{ V}$$

$$V_{ac} = V_a - V_c = 11.01 \text{ V} - 0 = 11.01 \text{ V}$$

9.)

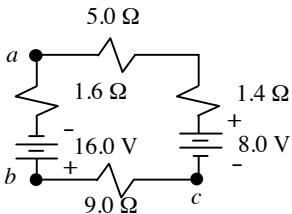

a.) Kirchoff's Loop rule:

 Going counterclockwise starting at  $a$ 

$$-V_{1.6\Omega} + V_{16\text{V}} - V_{9.0\Omega} + V_{8\text{V}} - V_{1.4\Omega} - V_{5.0\Omega} = 0$$

$$-I(1.6 \Omega) + 16 \text{ V} - I(9.0 \Omega) + 8.0 \text{ V} - I(1.4 \Omega) - I(5.0 \Omega) = 0$$

$$24 \text{ V} - I(17 \Omega) = 0 \quad \text{and} \quad I = \frac{24 \text{ V}}{17 \Omega} = 1.41 \text{ A} \quad \text{and is counterclockwise}$$

b.)  $V_{ab} = \mathcal{E} - Ir = 16.0 \text{ V} - (1.41 \text{ A})(1.6 \Omega) = 13.74 \text{ V}$

 c.)  $V_{ac} = V_a - V_c$  making point  $c$  the reference point (i.e.  $V_c = 0$ ).

$$V_a = I(9.0 \Omega) - 16 \text{ V} + I(1.6 \Omega) = (1.41 \text{ A})(10.6 \Omega) - 16 \text{ V} = -1.05 \text{ V}$$

$$V_{ac} = V_a - V_c = -1.05 \text{ V} - 0 = -1.05 \text{ V}$$

 10.)  $P = 369 \text{ W}$  and  $V = 18.0 \text{ V}$ 


$$P = IV = \frac{V}{R} V = \frac{V^2}{R} \quad \text{so} \quad R = \frac{V^2}{P} = \frac{(18 \text{ V})^2}{369 \text{ W}} = 0.878 \Omega$$

 11.)  $V = 12.0 \text{ V}$  and  $I = 0.29 \text{ A}$ 


$$P = IV \quad \text{and} \quad E = Pt = IVt = (0.29 \text{ A})(12 \text{ V})(16,200 \text{ s}) = 5.64 \times 10^4 \text{ J}$$

$$t = 4.5 \text{ hr} = 16,200 \text{ s}$$

HO 37 Solutions

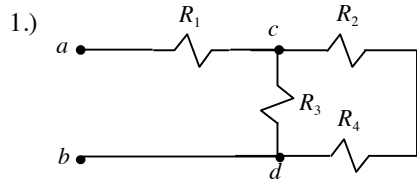


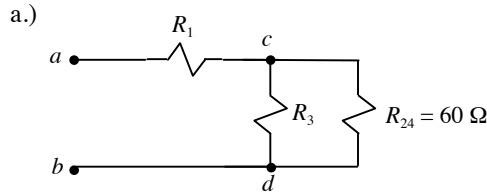$R_1 = 12 \Omega$ ,  $R_2 = 20.0 \Omega$ ,  $R_3 = 30.0 \Omega$ , and  $R_4 = 40.0 \Omega$ . The potential difference between  $a$  and  $b$  is  $96 \text{ V}$ .




$R_2$  and  $R_4$  are in series and can be replaced by their equivalent:
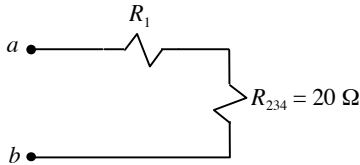
$$R_{24} = R_2 + R_4 = 20 \Omega + 40 \Omega = 60 \Omega$$




$R_{24}$  and  $R_3$  are in parallel and can be replaced by their equivalent:
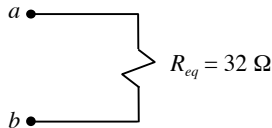
$$\frac{1}{R_{234}} = \frac{1}{R_{24}} + \frac{1}{R_3} = \frac{1}{60 \Omega} + \frac{1}{30 \Omega} \quad \text{and} \quad R_{234} = 20 \Omega$$



$R_{234}$  and  $R_1$  are in series and can be replaced by their equivalent:

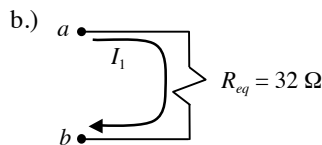
$$R_{eq} = R_{1234} = R_1 + R_{234} = 12 \Omega + 20 \Omega = 32 \Omega$$



The current coming out of the battery is:  $I_1 = \frac{V_{ab}}{R_{eq}} = \frac{96 \text{ V}}{32 \Omega} = 3 \text{ A}$


This is the current through  $R_1$  and the equivalent  $R_{234}$ . Also,
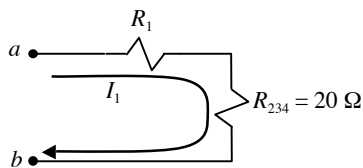
$$V_1 = I_1 R_1 = (3 \text{ A})(12 \Omega) = 36 \text{ V} \quad \text{and} \quad V_{234} = I_1 R_{234} = (3 \text{ A})(20 \Omega) = 60 \text{ V}$$




The voltage across  $R_3$  and the equivalent  $R_{24}$  is the same as that across their equivalent  $R_{234}$  because they are in parallel.
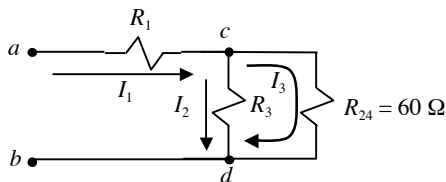
$$\text{So, } V_3 = V_{24} = V_{234} = 60 \text{ V}$$



$$\text{Also, } I_2 = \frac{V_3}{R_3} = \frac{60 \text{ V}}{30 \Omega} = 2 \text{ A} \quad \text{and} \quad I_3 = \frac{V_{24}}{R_{24}} = \frac{60 \text{ V}}{60 \Omega} = 1 \text{ A}$$
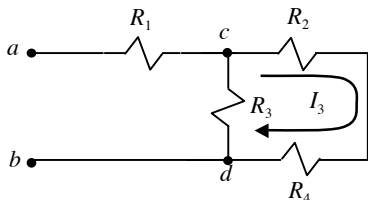
$$\text{(Note that } I_1 = I_2 + I_3 \text{)}$$



Finally,  $I_3$  is the current in  $R_2$  and  $R_4$  because they are in series and have the same current as their equivalent.

$$\text{and } V_2 = I_3 R_2 = (1 \text{ A})(20 \Omega) = 20 \text{ V}$$

$$V_4 = I_3 R_4 = (1 \text{ A})(40 \Omega) = 40 \text{ V}$$

$$\text{(Note that } V_{24} = V_2 + V_4 \text{)}$$

1.) b.) To summarize:


| Resistor | Resistance  | Current | Voltage | Power |
|----------|-------------|---------|---------|-------|
| $R_1$    | $12 \Omega$ | 3 A     | 36 V    | 108 W |
| $R_2$    | $20 \Omega$ | 1 A     | 20 V    | 20 W  |
| $R_3$    | $30 \Omega$ | 2 A     | 60 V    | 120 W |
| $R_4$    | $40 \Omega$ | 1 A     | 40 V    | 40 W  |

c.)

$$P = I_1 V_{ab} = (3 \text{ A})(96 \text{ V}) = 288 \text{ W}$$

This is same as the sum of the individual powers for each resistor.

2.)

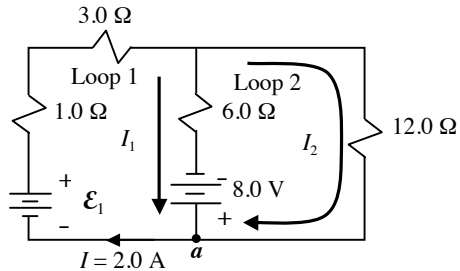

a.) Applying Kirchhoff's Loop Rule to Loop 1,

$$\mathcal{E}_1 + 8 \text{ V} = (2 \text{ A})(1 \Omega) + (2 \text{ A})(3 \Omega) + I_1(6 \Omega) \quad (1)$$

Applying Kirchhoff's Loop Rule to Loop 2,

$$8 \text{ V} = I_1(6 \Omega) - I_2(12 \Omega) \quad (2)$$

Applying Kirchhoff's Junction Rule to node  $a$ ,

$$I_1 + I_2 = I \quad \text{or} \quad I_2 = 2 \text{ A} - I_1 \quad (3)$$

Combining equations (2) and (3):  $8 \text{ V} = I_1(6 \Omega) - (2 \text{ A} - I_1)(12 \Omega) = -24 \text{ V} + I_1(18 \Omega)$

$$32 \text{ V} = I_1(18 \Omega) \quad \text{and} \quad I_1 = \frac{32 \text{ V}}{18 \Omega} = 1.78 \text{ A}$$

Substituting this into (1):

$$\mathcal{E}_1 + 8 \text{ V} = (2 \text{ A})(1 \Omega) + (2 \text{ A})(3 \Omega) + (1.78 \text{ A})(6 \Omega) = 18.67 \text{ V}$$

$$\mathcal{E}_1 = 18.67 \text{ V} - 8 \text{ V} = \boxed{10.67 \text{ V}}$$

b.)  $I_2 = 2 \text{ A} - I_1 = 2 \text{ A} - 1.78 \text{ A} = \boxed{0.22 \text{ A}}$

c.)  $P_{1\Omega} = IV = I^2R = (2 \text{ A})^2(1 \Omega) = \boxed{4 \text{ W}}$

$$P_{3\Omega} = IV = I^2R = (2 \text{ A})^2(3 \Omega) = \boxed{12 \text{ W}}$$

$$P_{6\Omega} = IV = I^2R = (1.78 \text{ A})^2(6 \Omega) = \boxed{19 \text{ W}}$$

$$P_{12\Omega} = IV = I^2R = (0.22 \text{ A})^2(12 \Omega) = \boxed{0.58 \text{ W}}$$


d.)  $P_{10.67\text{V}} = IV = (2 \text{ A})(10.67 \text{ V}) = \boxed{21.34 \text{ W}}$

$$P_{8\text{V}} = IV = (1.78 \text{ A})(8 \text{ V}) = \boxed{14.24 \text{ W}}$$

Power from batteries is:  $P_{batteries} = P_{10.67\text{V}} + P_{8\text{V}} = 21.34 \text{ W} + 14.24 \text{ W} = \boxed{35.6 \text{ W}}$

Power dissipated in resistors:  $P_{resistors} = P_{1\Omega} + P_{3\Omega} + P_{6\Omega} + P_{12\Omega} = 4 \text{ W} + 12 \text{ W} + 19 \text{ W} + 0.58 \text{ W} = \boxed{35.6 \text{ W}}$

HO 37 Solutions

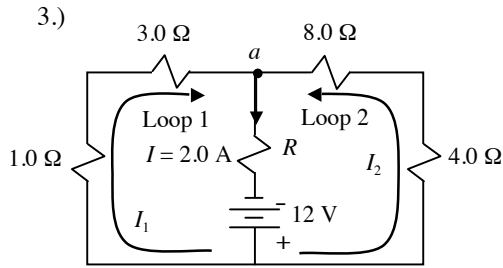

a.) Applying Kirchhoff's Loop Rule to Loop 1:

$$12 \text{ V} = I_1(1 \Omega) + I_1(3 \Omega) + (2 \text{ A})R = I_1(4 \Omega) + (2 \text{ A})R \quad (1)$$

Applying Kirchhoff's Loop Rule to Loop 2:

$$12 \text{ V} = I_2(8 \Omega) + I_2(4 \Omega) + (2 \text{ A})R = I_2(12 \Omega) + (2 \text{ A})R \quad (2)$$

Applying Kirchhoff's Junction Rule to node  $a$ ,

$$I_1 + I_2 = I = 2 \text{ A} \quad (3)$$

Subtracting equation (1) from equation (2):  $0 = I_2(12 \Omega) - I_1(4 \Omega) = 3I_2 - I_1 \quad (4)$

Combining equation (3) and (4):  $2 \text{ A} = 4I_2$  and  $I_2 = \frac{2 \text{ A}}{4} = 0.5 \text{ A}$  and  $I_1 = I - I_2 = 2 \text{ A} - 0.5 \text{ A} = 1.5 \text{ A}$

Returning to equation (1):  $12 \text{ V} = I_1(4 \Omega) + (2 \text{ A})R = (1.5 \text{ A})(4 \Omega) + (2 \text{ A})R = 6 \text{ V} + (2 \text{ A})R$

$$R = \frac{(12 \text{ V} - 6 \text{ V})}{(2 \text{ A})} = \boxed{3 \Omega}$$

b.) Found currents in part (a). Voltages are:

$$V_{1\Omega} = I_1 R = (1.5 \text{ A})(1 \Omega) = 1.5 \text{ V} \quad V_{3\Omega} = I_1 R = (1.5 \text{ A})(3 \Omega) = 4.5 \text{ V}$$

$$V_{8\Omega} = I_2 R = (0.5 \text{ A})(8 \Omega) = 4 \text{ V} \quad V_{4\Omega} = I_2 R = (0.5 \text{ A})(4 \Omega) = 2 \text{ V} \quad V_R = IR = (2 \text{ A})(3 \Omega) = 6 \text{ V}$$

To summarize:

| Resistance | Current | Voltage |
|------------|---------|---------|
| 3 $\Omega$ | 2 A     | 6 V     |
| 1 $\Omega$ | 1.5 A   | 1.5 V   |
| 3 $\Omega$ | 1.5 A   | 4.5 V   |
| 8 $\Omega$ | 0.5 A   | 4 V     |
| 4 $\Omega$ | 0.5 A   | 2 V     |

a.) (Again)


Currents can easily be obtained by recognizing that  $I_1$  and  $I_2$  are in parallel branches and divide the current  $I$ .

$$I_1 = \left( \frac{R_2}{R_1 + R_2} \right) I = \left( \frac{12 \Omega}{4 \Omega + 12 \Omega} \right) (2 \text{ A}) = 1.5 \text{ A}$$

$$I_2 = \left( \frac{R_1}{R_1 + R_2} \right) I = \left( \frac{4 \Omega}{4 \Omega + 12 \Omega} \right) (2 \text{ A}) = 0.5 \text{ A}$$

( $R_1$  is the total resistance of branch 1 and  $R_2$  is the total resistance of branch 2.)

HO 37 Solutions

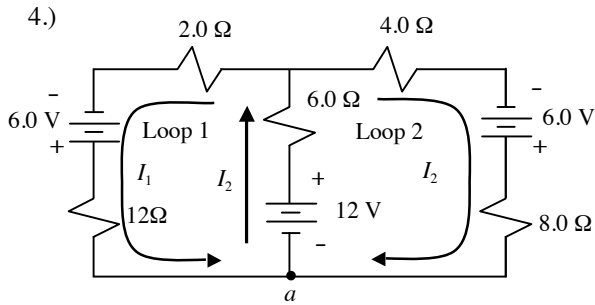

a.) Applying Kirchoff's Loop Rule to Loop 1:

$$6 \text{ V} + 12 \text{ V} = (12 \Omega + 2 \Omega)I_1 + (6 \Omega)I_2$$

$$18 \text{ V} = (14 \Omega)I_1 + (6 \Omega)I_2 \quad (1)$$

Applying Kirchoff's Loop Rule to Loop 2:

$$6 \text{ V} + 12 \text{ V} = (6 \Omega)I_2 + (4 \Omega + 8 \Omega)I_3$$

$$18 \text{ V} = (6 \Omega)I_2 + (12 \Omega)I_3 \quad (2)$$

Applying Kirchoff's Junction Rule to node  $a$ ,

$$I_1 + I_3 = I_2 \quad (3) \text{ so } I_3 = I_2 - I_1 \quad (3^*) \text{ and substituting this into equation (2) gives:}$$

$$18 \text{ V} = (6 \Omega)I_2 + (12 \Omega)(I_2 - I_1)$$

$$18 \text{ V} = (-12 \Omega)I_1 + (18 \Omega)I_2 \quad (2^*)$$

$$\text{Multiplying equation (1) by 3 gives:} \quad 54 \text{ V} = (42 \Omega)I_1 + (18 \Omega)I_2 \quad (1^*)$$

$$\text{and subtracting equation (2}^*) \text{ from (1}^*) \text{ gives: } 36 \text{ V} = (54 \Omega)I_1 \quad \text{and} \quad I_1 = \frac{36 \text{ V}}{54 \Omega} = 0.67 \text{ A}$$

$$\text{From equation (1}^*): \quad I_2 = \frac{18 \text{ V} + (12 \Omega)I_1}{18 \Omega} = \frac{18 \text{ V} + (12 \Omega)(0.67 \text{ A})}{18 \Omega} = 1.45 \text{ A}$$

$$\text{Finally, from (3}^*): \quad I_3 = I_2 - I_1 = 1.45 \text{ A} - 0.67 \text{ A} = 0.78 \text{ A}$$

Voltages are:

$$V_{2\Omega} = I_1 R = (0.67 \text{ A})(2 \Omega) = 1.34 \text{ V} \quad V_{12\Omega} = I_1 R = (0.67 \text{ A})(12 \Omega) = 8 \text{ V}$$

$$V_{4\Omega} = I_2 R = (0.78 \text{ A})(4 \Omega) = 3.12 \text{ V} \quad V_{8\Omega} = I_2 R = (0.78 \text{ A})(8 \Omega) = 6.24 \text{ V} \quad V_{6\Omega} = I_2 R = (1.45 \text{ A})(6 \Omega) = 8.7 \text{ V}$$

To summarize:

| Resistance | Current | Voltage |
|------------|---------|---------|
| 2 Ω        | 0.67 A  | 1.34 V  |
| 12 Ω       | 0.67 A  | 8 V     |
| 4 Ω        | 0.78 A  | 3.12 V  |
| 8 Ω        | 0.78 A  | 6.24 V  |
| 6 Ω        | 1.45 A  | 8.7 V   |


b.)

$$P_{6\text{V}} = I_1 V = (0.67 \text{ A})(6 \text{ V}) = \boxed{4 \text{ W}}$$

$$P_{6\text{V}} = I_2 V = (0.78 \text{ A})(6 \text{ V}) = \boxed{4.7 \text{ W}}$$

$$P_{12\text{V}} = IV = (1.45 \text{ A})(12 \text{ V}) = \boxed{17.4 \text{ W}}$$

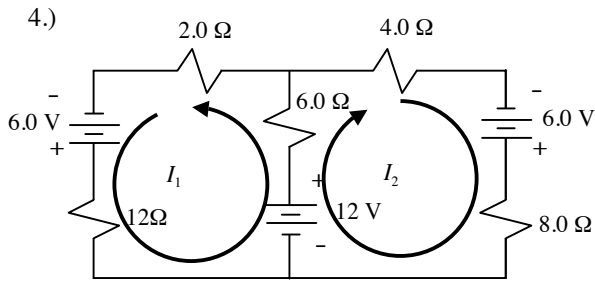Alternative solution using Mesh Currents:



a.) Using Loop Method (Mesh Currents):

$$12 \text{ V} + 6 \text{ V} = (20 \ \Omega)I_1 + (6 \ \Omega)I_2 \text{ (Loop 1)}$$

$$18 \text{ V} = (20 \ \Omega)I_1 + (6 \ \Omega)I_2 \text{ (1)}$$

$$18 \text{ V} = (6 \ \Omega)I_1 + (18 \ \Omega)I_2 \text{ (2) (Loop 2)}$$

Multiplying equation (1) by (3) gives:  $54 \text{ V} = (60 \ \Omega)I_1 + (18 \ \Omega)I_2$

and subtracting equation (2) gives:  $36 \text{ V} = (54 \ \Omega)I_1$  and  $I_1 = \frac{36 \text{ V}}{54 \ \Omega} = 0.67 \text{ A}$

From equation (1):  $3 \text{ A} = 3.33I_1 + I_2$  and  $I_2 = 3 \text{ A} - 3.33I_1 = 3 \text{ A} - 3.33(0.67 \text{ A}) = 0.78 \text{ A}$

$I_1$  is the current in the  $2 \ \Omega$  and  $12 \ \Omega$  resistors.

$I_2$  is the current in the  $4 \ \Omega$  and  $8 \ \Omega$  resistors.

$I_1 + I_2 = 1.45 \text{ A}$  is the current in the  $6 \ \Omega$  resistor.

Voltages are:

$$V_{2\Omega} = I_1 R = (0.67 \text{ A})(2 \ \Omega) = 1.34 \text{ V} \quad V_{12\Omega} = I_1 R = (0.67 \text{ A})(12 \ \Omega) = 8 \text{ V}$$

$$V_{4\Omega} = I_2 R = (0.78 \text{ A})(4 \ \Omega) = 3.12 \text{ V} \quad V_{8\Omega} = I_2 R = (0.78 \text{ A})(8 \ \Omega) = 6.24 \text{ V} \quad V_{6\Omega} = IR = (1.45 \text{ A})(6 \ \Omega) = 8.7 \text{ V}$$

To summarize:

| Resistance    | Current          | Voltage          |
|---------------|------------------|------------------|
| $2 \ \Omega$  | $0.67 \text{ A}$ | $1.34 \text{ V}$ |
| $12 \ \Omega$ | $0.67 \text{ A}$ | $8 \text{ V}$    |
| $4 \ \Omega$  | $0.78 \text{ A}$ | $3.12 \text{ V}$ |
| $8 \ \Omega$  | $0.78 \text{ A}$ | $6.24 \text{ V}$ |
| $6 \ \Omega$  | $1.45 \text{ A}$ | $8.7 \text{ V}$  |


b.)

$$P_{6\text{V}} = I_1 V = (0.67 \text{ A})(6 \text{ V}) = \boxed{4 \text{ W}}$$

$$P_{6\text{V}} = I_2 V = (0.78 \text{ A})(6 \text{ V}) = \boxed{4.7 \text{ W}}$$

$$P_{12\text{V}} = IV = (1.45 \text{ A})(12 \text{ V}) = \boxed{17.4 \text{ W}}$$

5.)

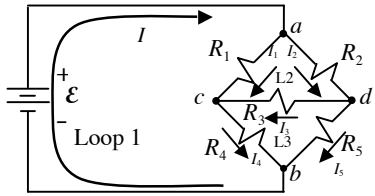

$R_1 = R_2 = R_3 = R_4 = 1.0 \Omega$ , and  $R_5 = 2.0 \Omega$ .  
The voltage across the battery is 13 V and it has no internal resistance.

a.)

Applying Kirchhoff's Loop rule on Loop 1:

$$\mathcal{E} = I_1 R_1 + I_4 R_4 \quad \text{or} \quad 13 \text{ V} = I_1(1 \Omega) + I_4(1 \Omega) \quad (1)$$

Applying Kirchhoff's Loop rule on Loop 2:

$$0 = I_1 R_1 - I_3 R_3 - I_2 R_2 \quad \text{or} \quad 0 = I_1(1 \Omega) - I_2(1 \Omega) - I_3(1 \Omega) \quad (2)$$

Applying Kirchhoff's Loop rule on Loop 3:

$$0 = I_3 R_3 + I_4 R_4 - I_5 R_5 \quad \text{or} \quad 0 = I_3(1 \Omega) + I_4(1 \Omega) + I_5(2 \Omega) \quad (3)$$

Applying Kirchhoff's Junction rule on junction a:

$$I = I_1 + I_2 \quad \text{and} \quad 0 = I - I_1 - I_2 \quad (4)$$

Applying Kirchhoff's Junction rule on junction c:

$$I_1 + I_3 = I_4 \quad \text{and} \quad 0 = I_1 + I_3 - I_4 \quad (5)$$

Applying Kirchhoff's Junction rule on junction d:

$$I_2 = I_3 + I_5 \quad \text{and} \quad 0 = I_2 - I_3 - I_5 \quad (6)$$

We have six equations with six unknowns. Setting up a matrix gives:

$$\begin{bmatrix} 0 & 1 \Omega & 0 & 0 & 1 \Omega & 0 \\ 0 & 1 \Omega & -1 \Omega & -1 \Omega & 0 & 0 \\ 0 & 0 & 0 & 1 \Omega & 1 \Omega & -2 \Omega \\ 1 & -1 & -1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & -1 & 0 & -1 \end{bmatrix} \cdot \begin{bmatrix} I \\ I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{bmatrix} = \begin{bmatrix} 13 \text{ V} \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

using matrix operations on a calculator:  $I = 11 \text{ A}$ ,  $I_1 = 6 \text{ A}$ ,  $I_2 = 5 \text{ A}$ ,  $I_3 = 1 \text{ A}$ ,  $I_4 = 7 \text{ A}$ , and  $I_5 = 4 \text{ A}$

| Resistor | Resistance | Current | Voltage |
|----------|------------|---------|---------|
| $R_1$    | $1 \Omega$ | 6 A     | 6 V     |
| $R_2$    | $1 \Omega$ | 5 A     | 5 V     |
| $R_3$    | $1 \Omega$ | 1 A     | 1 V     |
| $R_4$    | $1 \Omega$ | 7 A     | 7 V     |
| $R_5$    | $2 \Omega$ | 4 A     | 8 V     |




HO 37 Solutions

- b.) The equivalent resistance is found using the current ( $I$ ) from the battery. (Nothing is in parallel or series so ordinary methods for finding equivalent resistance will not work.)

$$V = IR \quad \text{and} \quad \mathcal{E} = IR_{eq} \quad \text{so} \quad R_{eq} = \frac{\mathcal{E}}{I} = \frac{13 \text{ V}}{11 \text{ A}} = \boxed{1.18 \Omega}$$

(Solution using Mesh Currents)

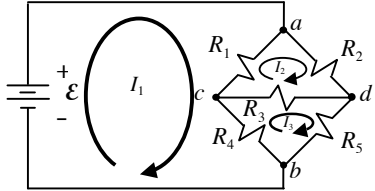

$$R_1 = R_2 = R_3 = R_4 = 1.0 \Omega, \text{ and } R_5 = 2.0 \Omega.$$

The voltage across the battery is 13 V and it has no internal resistance.

a.)

Applying Kirchhoff's Loop rule on Loop 1 (the loop containing  $I_1$ ):

$$\mathcal{E} = I_1(R_1 + R_4) - I_2R_1 - I_3R_4 \quad \text{or} \quad 13 \text{ V} = I_1(2 \Omega) - I_2(1 \Omega) - I_3(1 \Omega) \quad (1)$$

Applying Kirchhoff's Loop rule on Loop 2 (the loop containing  $I_2$ ):

$$0 = -I_1R_1 + I_2(R_1 + R_2 + R_3) - I_3R_3 \quad \text{or} \quad 0 = -I_1(1 \Omega) + I_2(3 \Omega) - I_3(1 \Omega) \quad (2)$$

Applying Kirchhoff's Loop rule on Loop 3 (the loop containing  $I_3$ ):

$$0 = -I_1R_4 - I_2R_3 + I_3(R_3 + R_4 + R_5) \quad \text{or} \quad 0 = -I_1(1 \Omega) - I_2(1 \Omega) + I_3(4 \Omega) \quad (3)$$

We have three equations with three unknowns. Setting up a matrix gives:

$$\begin{bmatrix} 2 \Omega & -1 \Omega & -1 \Omega \\ -1 \Omega & 3 \Omega & -1 \Omega \\ -1 \Omega & -1 \Omega & 4 \Omega \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 13 \text{ V} \\ 0 \\ 0 \end{bmatrix}$$

using matrix operations on a calculator:  $I_1 = 11 \text{ A}$ ,  $I_2 = 5 \text{ A}$ , and  $I_3 = 4 \text{ A}$

for  $R_1$  the current through it is  $I_1 - I_2 = 11 \text{ A} - 5 \text{ A} = 6 \text{ A}$


for  $R_2$  the current through it is  $I_2 = 5 \text{ A}$

for  $R_3$  the current through it is  $I_2 - I_3 = 5 \text{ A} - 4 \text{ A} = 1 \text{ A}$

for  $R_4$  the current through it is  $I_1 - I_3 = 11 \text{ A} - 4 \text{ A} = 7 \text{ A}$

for  $R_5$  the current through it is  $I_3 = 4 \text{ A}$

6.)

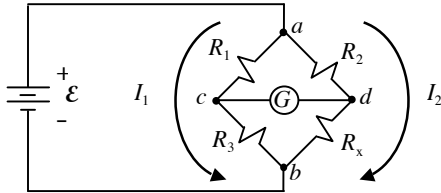

With no current through the galvanometer, the current through  $R_1$  and  $R_3$  is the same and equal to  $I_1$ .

Also, the current through  $R_2$  and  $R_x$  is the same and equal to  $I_2$ .

The potential at point  $c$  is the same as the potential at point  $d$  (There is no current through the meter, therefore there is no voltage drop since  $V_G = I_G R_G = 0$ ). Therefore,  $V_{ac} = V_{ad}$  and  $V_{cb} = V_{db}$ .

Using Ohm's Law:

$$\text{for } R_1 \quad V_{R1} = V_{ac} = I_1 R_1 \quad \text{and for } R_2 \quad V_{R2} = V_{ad} = I_2 R_2$$

$$\text{since } V_{ac} = V_{ad} \text{ it follows that } I_1 R_1 = I_2 R_2 \quad \text{or} \quad I_1 = I_2 \frac{R_2}{R_1} \quad (1)$$


$$\text{for } R_3 \quad V_{R3} = V_{cb} = I_1 R_3 \quad \text{and for } R_x \quad V_{Rx} = V_{db} = I_2 R_x$$

$$\text{since } V_{cb} = V_{db} \text{ it follows that } I_1 R_3 = I_2 R_x \quad \text{or} \quad I_1 = I_2 \frac{R_x}{R_3} \quad (2)$$

$$\text{Comparing equations 1 and 2 it follows that: } I_2 \frac{R_2}{R_1} = I_2 \frac{R_x}{R_3} \quad \text{and} \quad \frac{R_2}{R_1} = \frac{R_x}{R_3}$$

$$\text{Therefore: } R_x = \frac{R_2 R_3}{R_1}$$

Method 2:

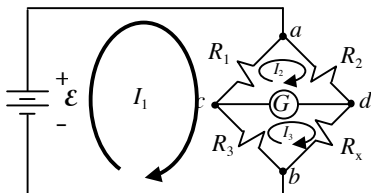

When bridge is balanced there is no current through the galvanometer.

$$\text{Therefore: } I_2 = I_3$$

Applying Kirchhoff's Loop rule on Loop 2 (the loop containing  $I_2$ ):

$$0 = -I_1 R_1 + I_2 (R_1 + R_2) \quad (1)$$

Applying Kirchhoff's Loop rule on Loop 3 (the loop containing  $I_3$ ):

$$0 = -I_1 R_3 + I_3 (R_3 + R_x) = -I_1 R_3 + I_2 (R_3 + R_x) \quad (2)$$


$$\text{From equation 1 it follows that: } I_2 = \frac{I_1 R_1}{(R_1 + R_2)} \quad \text{and from equation 2 it follows that: } I_2 = \frac{I_1 R_3}{(R_3 + R_x)}$$

$$\text{Therefore: } \frac{I_1 R_1}{(R_1 + R_2)} = \frac{I_1 R_3}{(R_3 + R_x)} \quad \text{and} \quad R_1 (R_3 + R_x) = R_3 (R_1 + R_2) \quad \text{and} \quad R_1 R_3 + R_1 R_x = R_3 R_1 + R_3 R_2$$


$$\text{so} \quad R_1 R_x = R_3 R_2 \quad \text{and} \quad R_x = \frac{R_3 R_2}{R_1}$$

Another look at Problem 3:

3.)

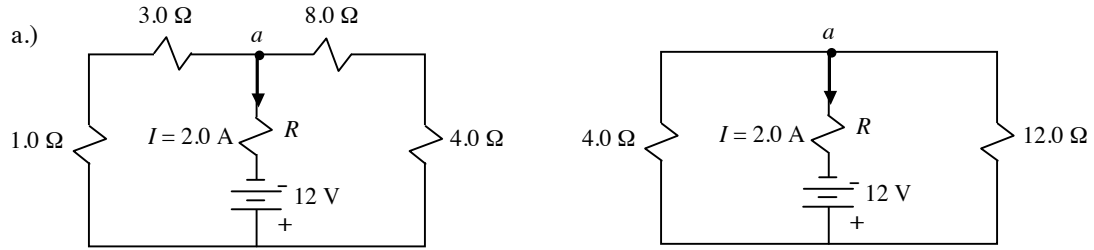

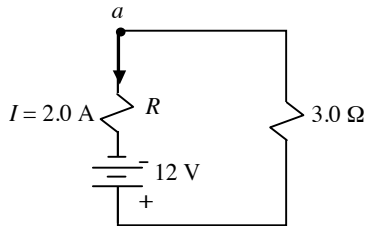The equivalent resistance for the entire circuit is:  $R_{eq} = \frac{V_{12V}}{I} = \frac{12\text{ V}}{2\text{ A}} = 6\ \Omega$




$$R_{eq} = R + 3\ \Omega = 6\ \Omega \quad \text{so} \quad R = 3\ \Omega$$

HO 38 Solutions

1.)  $R_{\text{coil}} = 50.0 \Omega, I_{fs} = 300 \mu\text{A}$

a.)

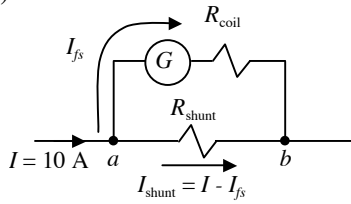


Ammeter reading 10 A full scale.

Voltage on  $R_{\text{coil}}$  and  $R_{\text{shunt}}$  are the same (they are parallel).

$$V_{\text{coil}} = V_{\text{shunt}} \quad \text{or} \quad I_{fs} R_{\text{coil}} = I_{\text{shunt}} R_{\text{shunt}} = (I - I_{fs}) R_{\text{shunt}}$$

$$R_{\text{shunt}} = \frac{I_{fs} R_{\text{coil}}}{(I - I_{fs})} = \frac{(300 \times 10^{-6} \text{ A})(50 \Omega)}{(10 \text{ A} - 300 \times 10^{-6} \text{ A})} = \boxed{1.5 \times 10^{-3} \Omega}$$

b.)

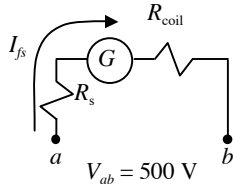


Voltmeter reading 500 V full scale.

$$V_{ab} = V_s + V_{\text{coil}} = I_{fs} R_s + I_{fs} R_{\text{coil}}$$

$$R_s = \frac{V_{ab} - I_{fs} R_{\text{coil}}}{I_{fs}} = \frac{(500 \text{ V} - (300 \times 10^{-6} \text{ A})(50 \Omega))}{(300 \times 10^{-6} \text{ A})} = \boxed{1.67 \times 10^6 \Omega}$$

2.)

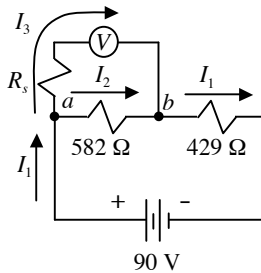

a.) Voltmeter reads 44.6 V so  $V_{ab} = 44.6 \text{ V}$ .

$$V_{ab} = I_2 R \quad \text{so} \quad I_2 = \frac{V_{ab}}{R} = \frac{44.6 \text{ V}}{582 \Omega} = 0.0766 \text{ A}$$

Applying Kirchhoff's Loop rule to loop with battery:


$$90 \text{ V} = 44.6 \text{ V} + I_1 (429 \Omega) \quad \text{and} \quad I_1 = \frac{(90 \text{ V} - 44.6 \text{ V})}{(429 \Omega)} = 0.1058 \text{ A}$$

At junction a:  $I_1 = I_2 + I_3$  or  $I_3 = I_1 - I_2 = 0.1058 \text{ A} - 0.0766 \text{ A} = 0.0292 \text{ A}$

Finally the meter is parallel to  $582 \Omega$  resistor and has same voltage.

$$V_{ab} = I_3 R_s \quad \text{and} \quad R_s = \frac{V_{ab}}{I_3} = \frac{44.6 \text{ V}}{0.0292 \text{ A}} = \boxed{1527 \Omega}$$

b.)

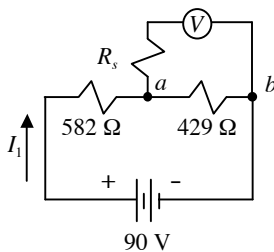

The meter resistance is parallel to  $429 \Omega$  resistor and their equivalent resistance is:


$$\frac{1}{R_{ab}} = \frac{1}{1527 \Omega} + \frac{1}{429 \Omega} \quad \text{and} \quad R_{ab} = 334.9 \Omega$$

This is in series with the  $582 \Omega$  resistor so their equivalent resistance is:

$$R_{eq} = 334.9 \Omega + 582 \Omega = 916.9 \Omega$$


$$\text{Also: } I_1 = \frac{V_{90\text{V}}}{R_{eq}} = \frac{90 \text{ V}}{916.9 \Omega} = 0.0982 \text{ A}$$

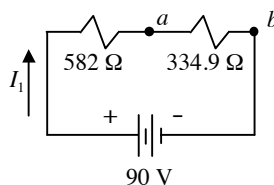The voltmeter reads  $V_{ab}$  and  $V_{ab} = I_1 R_{ab} = (0.0982 \text{ A})(334.9 \Omega) = \boxed{32.9 \text{ V}}$



HO 38 Solutions

3.)

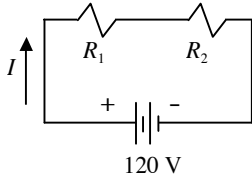

The meters will deflect full-scale when the voltage across them is 150 V:

For meter 1:  $I_{fs1} = \frac{V}{R_1} = \frac{150 \text{ V}}{15 \times 10^3 \Omega} = 0.01 \text{ A}$

For meter 2:  $I_{fs2} = \frac{V}{R_2} = \frac{150 \text{ V}}{150 \times 10^3 \Omega} = 0.001 \text{ A}$

The actual current through each is:  $I = \frac{V_{120V}}{R_1 + R_2} = \frac{120 \text{ V}}{(15 \times 10^3 \Omega + 150 \times 10^3 \Omega)} = 7.27 \times 10^{-4} \text{ A}$


Reading on each meter will be:  $V_{meter} = V_{fs} \left( \frac{I}{I_{fs}} \right)$

so  $V_{meter1} = V_{fs1} \left( \frac{I}{I_{fs1}} \right) = (150 \text{ V}) \left( \frac{7.27 \times 10^{-4} \text{ A}}{0.01 \text{ A}} \right) = \boxed{10.9 \text{ V}}$

(Note that the sum is 120 V)

and  $V_{meter2} = V_{fs2} \left( \frac{I}{I_{fs2}} \right) = (150 \text{ V}) \left( \frac{7.27 \times 10^{-4} \text{ A}}{0.001 \text{ A}} \right) = \boxed{109.1 \text{ V}}$

4.)

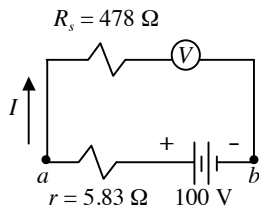


Applying Kirchhoff's Loop rule:  $V_{100V} = Ir + IR_s$

$$I = \frac{V_{100V}}{(r + R_s)} = \frac{100 \text{ V}}{(5.83 \Omega + 478 \Omega)} = 0.207 \text{ A}$$

The terminal voltage  $V_{ab}$  is:  $V_{ab} = V_{100V} - Ir = 100 \text{ V} - (0.207 \text{ A})(5.83 \Omega) = \boxed{98.8 \text{ V}}$

5.)

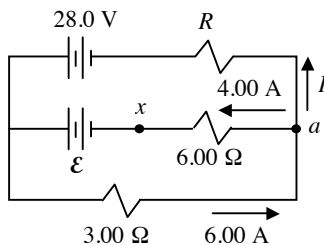

a.) Applying Kirchhoff's Junction rule at junction a:

$$6 \text{ A} = I + 4 \text{ A} \quad \text{so} \quad I = 6 \text{ A} - 4 \text{ A} = \boxed{2 \text{ A}}$$

b.) The 3 Ω resistor is parallel to the 28 V battery and R so they have the same voltage.


$$V_{3\Omega} = IR = (6 \text{ A})(3 \Omega) = 18 \text{ V} \quad \text{and} \quad V_{3\Omega} = V_{28V} - IR$$

Therefore:  $R = \frac{(V_{28V} - V_{3\Omega})}{I} = \frac{(28 \text{ V} - 18 \text{ V})}{2 \text{ A}} = \boxed{5 \Omega}$

c.) The 3 Ω resistor is also parallel to *emf*  $\mathcal{E}$  and the 6 Ω resistor so they have the same voltage.

$$V_{3\Omega} = \mathcal{E} - IR \quad \text{and} \quad \mathcal{E} = V_{3\Omega} + IR = 18 \text{ V} + (4 \text{ A})(6 \Omega) = \boxed{42 \text{ V}}$$


d.)

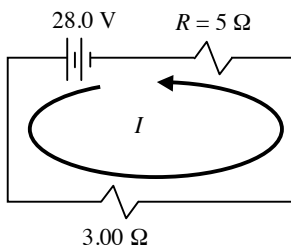


Applying Kirchhoff's Loop rule:  $V_{28V} = V_R + V_{3\Omega} = IR + IR_{3\Omega}$

$$I = \frac{V_{28V}}{(R + R_{3\Omega})} = \frac{28 \text{ V}}{(5 \Omega + 3 \Omega)} = 3.5 \text{ A}$$


HO 38 Solutions

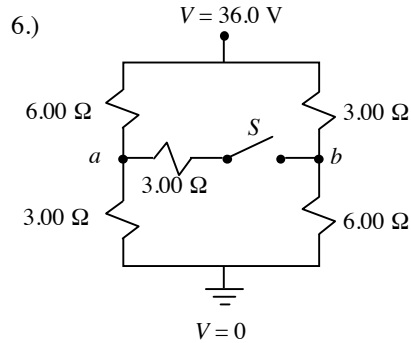

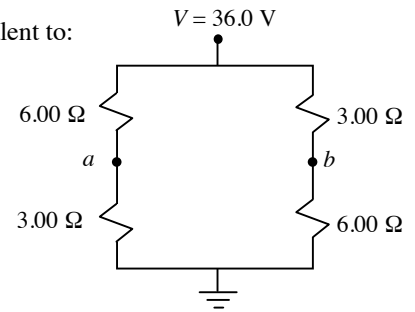
a.) With switch open the circuit is equivalent to:




This reduces to :

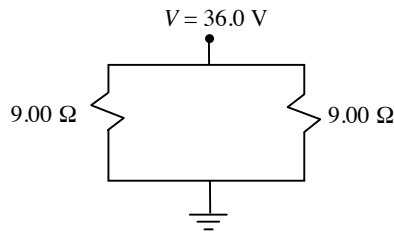

and finally:

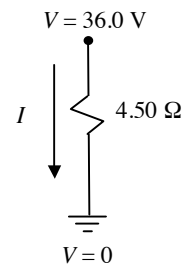

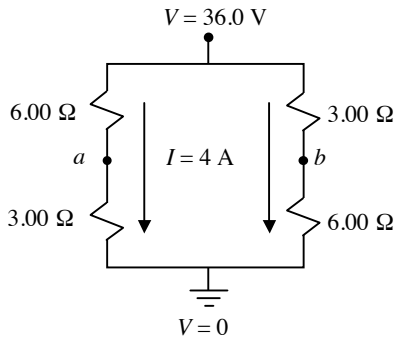The current from the battery is:  $I = \frac{V_{36V}}{R_{eq}} = \frac{36 \text{ V}}{4.5 \Omega} = 8 \text{ A}$  and this is split equally between the  $9 \Omega$  equivalents.





So:  $V_a = V_{36V} - V_{6\Omega} = V_{36V} - I_{6\Omega}R_{6\Omega} = 36 \text{ V} - (4 \text{ A})(6 \Omega) = 12 \text{ V}$

$V_b = V_{36V} - V_{3\Omega} = V_{36V} - I_{3\Omega}R_{3\Omega} = 36 \text{ V} - (4 \text{ A})(3 \Omega) = 24 \text{ V}$

It follows that:  $V_{ab} = V_a - V_b = 12 \text{ V} - 24 \text{ V} = \boxed{-12 \text{ V}}$

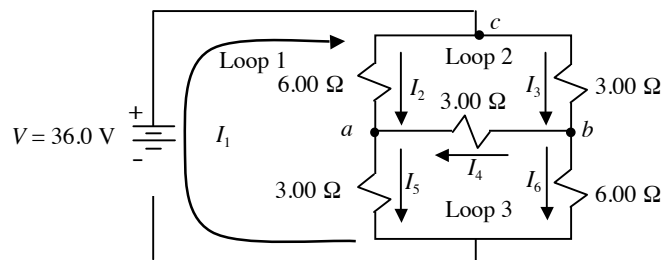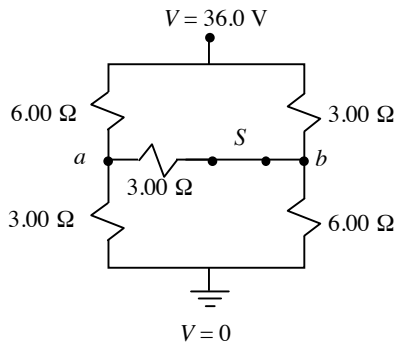b.) Closing the switch the circuit becomes:



The circuit is like the *bridge* circuit on HO 36 with nothing in parallel or series.

Applying Kirchhoff's Loop rule on Loop 1:

$$36 \text{ V} = I_2(6 \Omega) + I_5(3 \Omega) \quad (1)$$

Applying Kirchhoff's Loop rule on Loop 2:

$$0 = I_3(3 \Omega) + I_4(3 \Omega) - I_2(6 \Omega) \quad (2)$$

6.) b.)

Applying Kirchhoff's Loop rule on Loop 3:

$$0 = I_4(3 \Omega) + I_5(3 \Omega) - I_6(6 \Omega) \quad (3)$$

Applying Kirchhoff's Junction rule on junction c:

$$I_1 = I_2 + I_3 \text{ and } 0 = I_1 - I_2 - I_3$$

Applying Kirchhoff's Junction rule on junction a:

$$I_2 + I_4 = I_5 \text{ and } 0 = I_2 + I_4 - I_5$$

Applying Kirchhoff's Junction rule on junction b:

$$I_3 = I_4 + I_6 \text{ and } 0 = I_3 - I_4 - I_6$$

We have six equations with six unknowns. Setting up a matrix gives:

$$\begin{bmatrix} 0 & 6 \Omega & 0 & 0 & 3 \Omega & 0 \\ 0 & 0 & 0 & 3 \Omega & 3 \Omega & -6 \Omega \\ 0 & -6 \Omega & 3 \Omega & 3 \Omega & 0 & 0 \\ 1 & -1 & -1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & -1 & 0 & -1 \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \end{bmatrix} = \begin{bmatrix} 36 \text{ V} \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

using matrix operations on a calculator:  $I_1 = 8.57 \text{ A}$ ,  $I_2 = 3.43 \text{ A}$ ,  $I_3 = 5.14 \text{ A}$ ,  $I_4 = 1.71 \text{ A}$ ,  $I_5 = 5.14 \text{ A}$ , and  $I_6 = 3.43 \text{ A}$



The current through the switch is :  $I_{\text{switch}} = I_4 = \boxed{1.71 \text{ A}}$

c.) The equivalent resistance is found using the current ( $I_1$ ) from the battery. (Nothing is in parallel or series so ordinary methods for finding equivalent resistance will not work.)

$$V = IR \quad \text{and} \quad V_{36\text{V}} = I_1 R_{eq} \quad \text{so} \quad R_{eq} = \frac{V_{36\text{V}}}{I_1} = \frac{36 \text{ V}}{8.57 \text{ A}} = \boxed{4.20 \Omega}$$

(Solution using Mesh Currents)

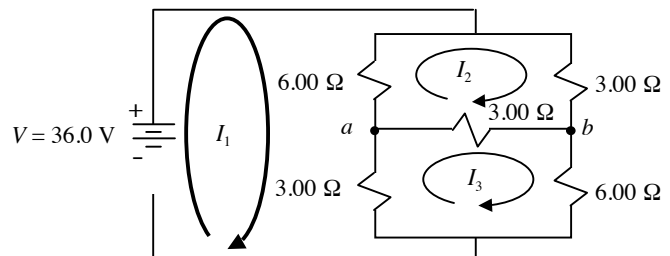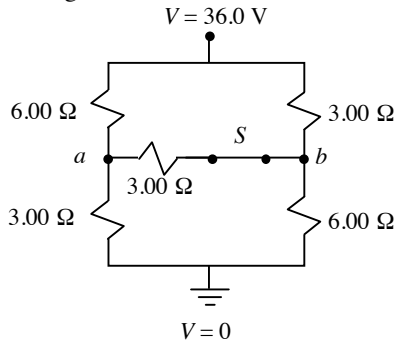b.) Closing the switch the circuit becomes:



The circuit is like the *bridge* circuit on HO 36 with nothing in parallel or series. Using Loop Method:

Applying Kirchhoff's Loop rule on Loop 1 (the loop containing  $I_1$ ):

$$36 \text{ V} = I_1(9 \Omega) - I_2(6 \Omega) - I_3(3 \Omega) \quad (1)$$

HO 38 Solutions

Applying Kirchhoff's Loop rule on Loop 2 (the loop containing  $I_2$ ):

$$0 = -I_1(6 \Omega) + I_2(12 \Omega) - I_3(3 \Omega) \quad (2)$$

Applying Kirchhoff's Loop rule on Loop 3 (the loop containing  $I_3$ ):

$$0 = -I_1(3 \Omega) - I_2(3 \Omega) + I_3(12 \Omega) \quad (3)$$


We have three equations with three unknowns. Setting up a matrix gives:

$$\begin{bmatrix} 9 \Omega & -6 \Omega & -3 \Omega \\ -6 \Omega & 12 \Omega & -3 \Omega \\ -3 \Omega & -3 \Omega & 12 \Omega \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 36 \text{ V} \\ 0 \\ 0 \end{bmatrix}$$

using matrix operations on a calculator:  $I_1 = 8.57 \text{ A}$ ,  $I_2 = 5.14 \text{ A}$ , and  $I_3 = 3.43 \text{ A}$

The current through the switch is :  $I_{\text{switch}} = I_2 - I_3 = 5.14 \text{ A} - 3.43 \text{ A} = \boxed{1.71 \text{ A}}$
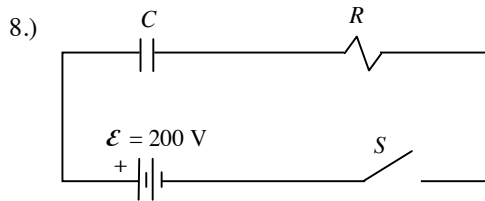
$$7.) \quad RC [=] \Omega \cdot \text{F} [=] \frac{\text{V C}}{\text{A V}} [=] \frac{\text{C}}{\left(\frac{\text{C}}{\text{s}}\right)} [=] \text{s}$$




At time  $t = 0$ ,  $I_o = 8.6 \times 10^{-4} \text{ A}$ ,  $Q_o = 0$ , and  $RC = 5.7 \text{ s} = \tau$ .

When switch is closed uncharged capacitor has no resistance and

$$\mathcal{E} = I_o R \quad \text{so} \quad R = \frac{\mathcal{E}}{I_o} = \frac{200 \text{ V}}{8.6 \times 10^{-4} \text{ A}} = \boxed{2.33 \times 10^5 \Omega}$$
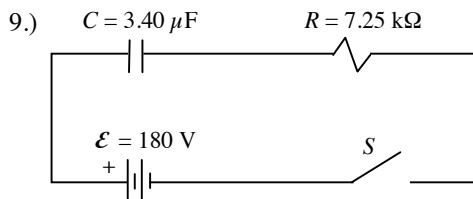
$$RC = \tau \quad \text{so} \quad C = \frac{\tau}{R} = \frac{5.7 \text{ s}}{2.33 \times 10^5 \Omega} = \boxed{2.45 \times 10^{-5} \text{ F}}$$



$Q_o = 0$

Find the time for the current to decay to  $i = 0.0185 \text{ A}$ .

$$\text{For charging:} \quad i(t) = I_o e^{-\frac{t}{RC}} = \frac{\mathcal{E}}{R} e^{-\frac{t}{RC}}$$

The time that the current is  $0.0185 \text{ A}$  is:

$$t = -RC \ln\left(\frac{Ri(t)}{\mathcal{E}}\right) = -(7.25 \times 10^3 \Omega)(3.4 \times 10^{-6} \text{ F}) \ln\left(\frac{(7.25 \times 10^3 \Omega)(0.0185 \text{ A})}{180 \text{ V}}\right) = 7.25 \times 10^{-3} \text{ s}$$

The charge on the capacitor is:

$$q(t) = Q_f \left(1 - e^{-\frac{t}{RC}}\right) = C\mathcal{E} \left(1 - e^{-\frac{t}{RC}}\right) = (3.4 \times 10^{-6} \text{ F})(180 \text{ V}) \left(1 - e^{-\frac{7.25 \times 10^{-3} \text{ s}}{(7.25 \times 10^3 \Omega)(3.4 \times 10^{-6} \text{ F})}}\right) = \boxed{1.56 \times 10^{-4} \text{ C}}$$



9.)

Method 2:


Realizing that the sum of the voltage on the capacitor and resistor must always be 180 V and at the time when  $i = 0.0185$  A:

$$v_R = iR = (0.0185 \text{ A})(7.25 \times 10^3 \Omega) = 134.1 \text{ V}$$

$$\mathcal{E} = v_R + v_C \quad \text{so} \quad v_C = \mathcal{E} - v_R = 180 \text{ V} - 134.1 \text{ V} = 45.9 \text{ V}$$

$$\text{The charge is } q_C = Cv_C = (3.4 \times 10^{-6} \text{ F})(45.9 \text{ V}) = 1.56 \times 10^{-4} \text{ C}$$

10.)

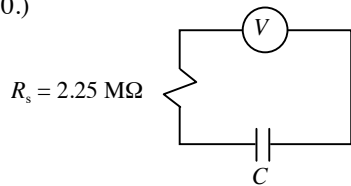

On capacitor  $V_o = 15$  V and after 5.00 s voltmeter reads 5.0 V.

The voltmeter reads the voltage on the capacitor so at  $t = 5$  s,  $v_C = 5.0$  V.



While discharging the voltage on the capacitor is:  $v(t) = V_o e^{-\frac{t}{RC}}$

Solving for C:


$$\ln\left(\frac{v(t)}{V_o}\right) = -\frac{t}{RC}$$

$$\text{so } C = \frac{-t}{R \ln\left(\frac{v(t)}{V_o}\right)} = \frac{-5 \text{ s}}{(2.25 \times 10^6 \Omega) \ln\left(\frac{5 \text{ V}}{15 \text{ V}}\right)} = \boxed{2.02 \times 10^{-6} \text{ F}}$$

HO 39 Solutions

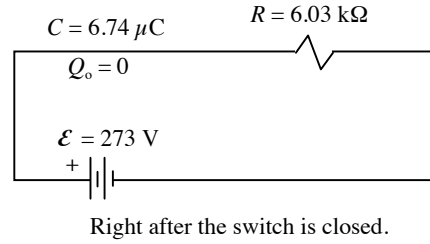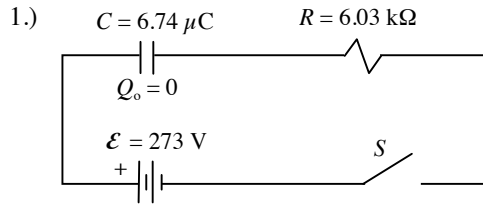

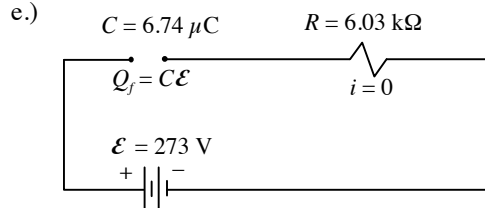
- a.) The capacitor is uncharged and  $v_C = \frac{Q}{C} = \boxed{0}$
- b.) The voltage across the resistor  $v_R = \mathcal{E} = \boxed{273 \text{ V}}$
- c.) The charge on the capacitor  $q = Q_0 = \boxed{0}$
- d.) The current through the resistor  $i_R = \frac{v_R}{R} = \frac{\mathcal{E}}{R} = \frac{273 \text{ V}}{6.03 \times 10^3 \Omega} = \boxed{0.0453 \text{ A}}$



- a.) The voltage across the capacitor  $v_C = \mathcal{E} = \boxed{273 \text{ V}}$
- b.) The voltage across the resistor  $v_R = iR = \boxed{0}$

A long time after the switch is closed.

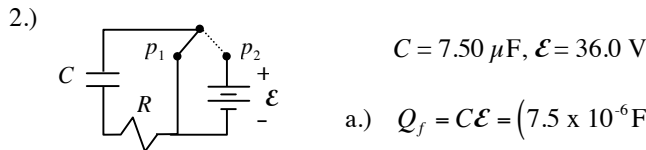- c.) The charge on the capacitor  $q = Q_f = C\mathcal{E} = (6.74 \times 10^{-6} \text{ F})(273 \text{ V}) = \boxed{1.84 \times 10^{-3} \text{ C}}$
- d.) The current through the resistor  $i_R = \boxed{0}$



a.)  $Q_f = C\mathcal{E} = (7.5 \times 10^{-6} \text{ F})(36 \text{ V}) = \boxed{2.7 \times 10^{-4} \text{ C}}$

b.)  $q(t) = Q_f \left(1 - e^{-\frac{t}{RC}}\right)$  so  $\ln\left(1 - \frac{q(t)}{Q_f}\right) = \frac{-t}{RC}$


and  $R = \frac{-t}{C \ln\left(1 - \frac{q(t)}{Q_f}\right)} = \frac{-(3 \times 10^{-3} \text{ s})}{(7.5 \times 10^{-6} \text{ F}) \ln\left(1 - \frac{(225 \times 10^{-6} \text{ C})}{(270 \times 10^{-6} \text{ C})}\right)} = \boxed{223 \Omega}$

c.)  $q(t) = Q_f \left(1 - e^{-\frac{t}{RC}}\right)$  so  $\ln\left(1 - \frac{q(t)}{Q_f}\right) = \frac{-t}{RC}$

and  $t = -RC \ln\left(1 - \frac{q(t)}{Q_f}\right) = -(223 \Omega)(7.5 \times 10^{-6} \text{ F}) \ln\left(1 - \frac{0.99Q_f}{Q_f}\right) = \boxed{7.70 \times 10^{-3} \text{ s}}$

HO 39 Solutions

3.)

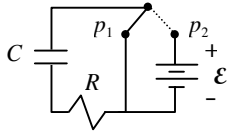

$$C = 40.0 \mu\text{F}, \mathcal{E} = 24.0 \text{ V}, \text{ and } R = 950 \Omega$$



$$\text{a.) } q(t) = Q_f \left(1 - e^{-\frac{t}{RC}}\right) = C\mathcal{E} \left(1 - e^{-\frac{t}{RC}}\right) = (40 \times 10^{-6} \text{ F})(24 \text{ V}) \left(1 - e^{-\frac{(0.05 \text{ s})}{(950 \Omega)(40 \times 10^{-6} \text{ F})}}\right) = \boxed{7.02 \times 10^{-4} \text{ C}}$$

$$\text{b.) } v_C = \frac{q}{C} = \frac{(7.02 \times 10^{-4} \text{ C})}{(40 \times 10^{-6} \text{ F})} = \boxed{17.6 \text{ V}} \quad \text{and} \quad \mathcal{E} = v_R + v_C \quad \text{or} \quad v_R = \mathcal{E} - v_C = 24 \text{ V} - 17.6 \text{ V} = \boxed{6.4 \text{ V}}$$

$$\text{c.) } v_C = \frac{q}{C} = \frac{(7.02 \times 10^{-4} \text{ C})}{(40 \times 10^{-6} \text{ F})} = \boxed{17.6 \text{ V}} \quad \text{and} \quad 0 = v_R + v_C \quad \text{or} \quad v_R = -v_C = \boxed{-17.6 \text{ V}}$$

$$\text{d.) } q(t) = Q_0 e^{-\frac{t}{RC}} = (7.02 \times 10^{-4} \text{ C}) e^{-\frac{(0.05 \text{ s})}{(950 \Omega)(40 \times 10^{-6} \text{ F})}} = \boxed{1.88 \times 10^{-4} \text{ C}}$$

4.)

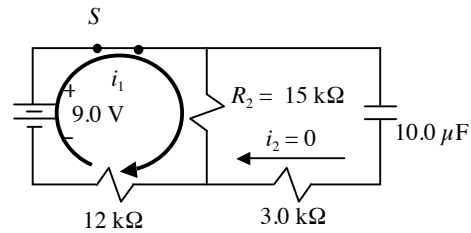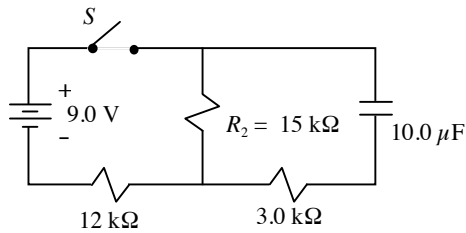

At steady state.

a.) At steady state the capacitor is fully charged and current has decayed to zero.

$$\text{The current through the } 3.0 \text{ k}\Omega \text{ resistor } \boxed{i_2 = 0}$$

The current through the 15 kΩ and the 12 kΩ resistors is the same since they are in series.

$$i_1 = \frac{V_{9V}}{R_{eq}} = \frac{9 \text{ V}}{(15,000 \Omega + 12,000 \Omega)} = \boxed{3.33 \times 10^{-4} \text{ A}}$$

b.) The voltage on the capacitor is the voltage on 15 kΩ resistor. (No voltage drop on 3 kΩ resistor.)

$$v_C = v_{R_2} = i_1 R_2 = (3.33 \times 10^{-4} \text{ A})(15,000 \Omega) = 5 \text{ V}$$

$$\text{The charge is: } q_C = C v_C = (10 \times 10^{-6} \text{ F})(5 \text{ V}) = \boxed{5.0 \times 10^{-5} \text{ C}}$$

c.) When the switch is open the capacitor discharges into the series combination of the 3 kΩ and 15 kΩ resistor.


$$i_2 = I_0 e^{-\frac{t}{R_{eq}C}} = \frac{v_C(0)}{R_{eq}} e^{-\frac{t}{R_{eq}C}} = \frac{5 \text{ V}}{(15,000 \Omega + 3000 \Omega)} e^{-\frac{t}{(15,000 \Omega + 3000 \Omega)(10 \times 10^{-6} \text{ F})}} = \boxed{(2.78 \times 10^{-4} \text{ A}) e^{-\frac{t}{(0.18 \text{ s})}}}$$

$$\text{d.) } q(t) = Q_0 e^{-\frac{t}{R_{eq}C}} \quad \text{so} \quad \ln\left(\frac{q(t)}{Q_0}\right) = \frac{-t}{R_{eq}C}$$


$$\text{and } t = -R_{eq}C \ln\left(\frac{q(t)}{Q_0}\right) = -(18,000 \Omega)(10 \times 10^{-6} \text{ F}) \ln\left(\frac{0.2Q_0}{Q_0}\right) = \boxed{0.29 \text{ s}}$$

HO 39 Solutions

5.)

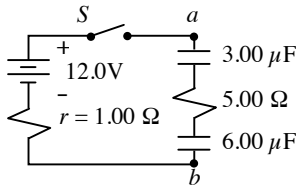

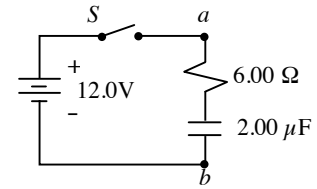The circuit is equivalent to:  
(resistors in series capacitors in series.)



a.) time constant is  $\tau = R_{eq}C_{eq} = (6 \Omega)(2 \times 10^{-6} \text{F}) = \boxed{1.2 \times 10^{-5} \text{s}}$

b.) The final charge on the  $3 \mu\text{C}$  capacitor is the same as the final charge on its equivalent.



$$Q_f = C_{eq}V = (2 \times 10^{-6} \text{F})(12 \text{V}) = 2.4 \times 10^{-5} \text{C}$$

The charge at any time is:  $q(t) = Q_f \left( 1 - e^{-\frac{t}{R_{eq}C_{eq}}} \right)$  (both capacitors have same charge at all times)

So the voltage on the  $3 \mu\text{C}$  capacitor at any time is:  $v(t) = \frac{Q_f}{C} \left( 1 - e^{-\frac{t}{R_{eq}C_{eq}}} \right)$

When  $t = \tau$  the voltage on the  $3 \mu\text{C}$  capacitor is:  $v(\tau) = \frac{(2.4 \times 10^{-5} \text{C})}{(3 \times 10^{-6} \text{F})} (1 - e^{-1}) = \boxed{5.06 \text{V}}$

6.)

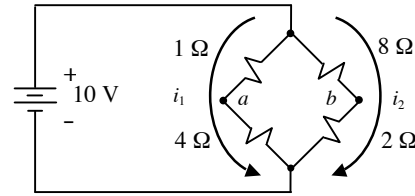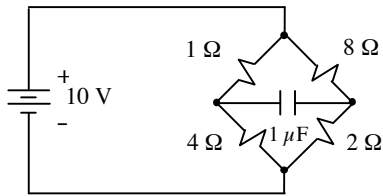

After a long time, capacitor is fully charged.




a.) When the capacitor is fully charged, no current passes through it.

$$i_1 = \frac{V}{R} = \frac{10 \text{V}}{(1 \Omega + 4 \Omega)} = 2 \text{A} \quad \text{and} \quad i_2 = \frac{V}{R} = \frac{10 \text{V}}{(8 \Omega + 2 \Omega)} = 1 \text{A}$$

$$V_a = V_{10V} - V_{1\Omega} = 10 \text{V} - (2 \text{A})(1 \Omega) = 8 \text{V} \quad \text{and} \quad V_b = V_{10V} - V_{8\Omega} = 10 \text{V} - (1 \text{A})(8 \Omega) = 2 \text{V}$$

The voltage on the capacitor is:  $V_a - V_b = 8 \text{V} - 2 \text{V} = \boxed{6 \text{V}}$

b.)

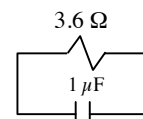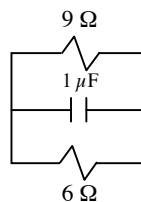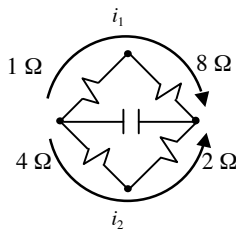

The equivalent circuit while discharging.

$$v(t) = V_0 e^{-\frac{t}{R_{eq}C}} \quad \text{or} \quad t = -R_{eq}C \ln \left( \frac{v(t)}{V_0} \right) = -(3.6 \Omega)(1 \times 10^{-6} \text{F}) \ln \left( \frac{0.1V_0}{V_0} \right) = \boxed{8.29 \times 10^{-6} \text{s}}$$